

Name:

Roll Number:

Laboratory 7

A: /4 B: /3 C: /6 D: /2 Tot: /15

Power transfer and impedance matching

/2

Bonus

Part A: DC Power transfer

Consider the circuit shown in Fig 1. It has an *ideal* DC voltage source V_S . A practical voltage source will always have some internal resistance, here denoted by R_S . The object in the dotted box containing a voltage source V_S with an internal resistance R_S supplying a current I is our model of a practical power source. R_L is the load resistance to which the power is supplied.

Using Kirchoff's laws, work out the following questions

Q1: What is the *total* power produced by the source? $P_{S|total}$?

/0.5

Q2: What is the power dissipated *inside* the source?

/0.5

Q3: What is the power dissipated in the load?

/0.5

Q4: Since you can specify the load R_L in your design (R_S is a fixed parameter of the power supply) what is value to which you must set R_L so as to ensure *maximum* transfer of power from source to load?

/0.5

Q5: Define efficiency of power transfer as the ratio of power dissipated in the load, to the total power produced by the source $\eta = P_L / P_{S|total}$ What is the efficiency of power transfer in Fig 1?

/0.5

Q6: What is the efficiency in the case of *maximum* power transfer that you have worked out in Q4?

/0.5


[Note that this intrinsic limit on the efficiency of power transfer from a DC source is the reason that power is transferred as AC from the source to your wall socket]

Q7: Consider the limiting case for efficiency of power transfer worked out in Q5 above:

Keeping R_S fixed, For what value of R_L would you get $\eta = 1$?

Think carefully! Although the efficiency is 1, is any power actually transferred in this case?(what would be the value of the current I in the circuit?)

/1

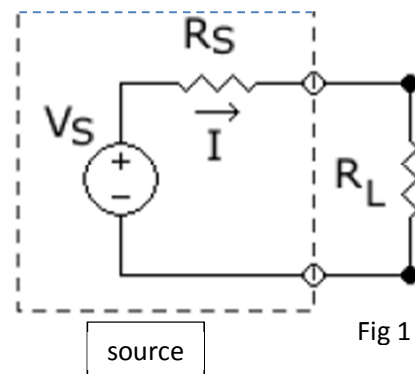

Name: _____

Roll Number: _____

Part B: AC power transfer

For most circuits in analog electronics, our goal is to transfer time-varying electrical signals from one part of the circuit to another without introducing distortions. The load of each part of the circuit must be modeled using complex impedances which take into account the frequency (hence time) dependence of the equivalent resistance presented by that part. Distortions in signal transfer typically occur in the form of *reflections*: A time-varying electronic signal travelling on a cable is an electromagnetic wave – when it reaches its destination (the load) some fraction of it can be reflected back to the source.

Fig 2 gives a simple analogy from physics:

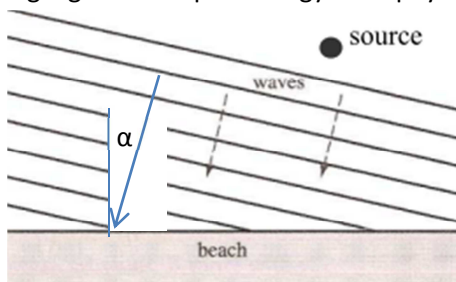



Fig 2: Example of impedance matching in waves arriving at a beach. The beach is the 'load'. The waves have a certain wavelength (distance between crests of the waves) and frequency. By 'adjusting' the beach's angle α with respect to the direction of arrival of the waves, the quantity of wave energy reflected back to the source can be controlled. The quantity of reflected wave energy goes as $\sim 1/\cos(\alpha)$. It is easy to see that for head-on incidence $\alpha=0$, the reflection is maximum. In case of reflections, the waves observed on the ocean surface (i.e. the medium, or in electronic terms – the cable) will be a superposition of the source wave and the reflections.

Experiment to measure reflections in coaxial cable

Our objective is to measure reflections (an electromagnetic wave) in a coaxial cable. The length of the cable is one of the parameters in our measurement.

Fig 3: cutaway sectional view of a coaxial cable.

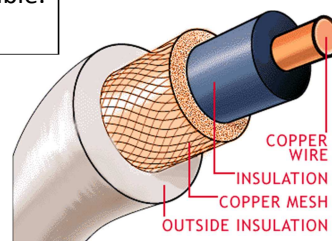Refer to Fig 4, where the cable of impedance Z_0 is explicitly put in as an intermediate circuit block (DeviceUnderTest = DUT) between the source and load



Definition:

The reflection coefficient Γ is defined as the *ratio* of the reflected signal to the total signal produced by the source. If the source produces voltage V_s and the reflected voltage is V_R , $\Gamma = V_R/V_s$


Note that each of the elements in the circuit of Fig 4, must obey Ohm's law: $Z = V/I$: this is useful in calculating Γ

Name: _____

Roll Number: _____

QB₁: Given a source of impedance Z_S and a cable of impedance Z_0 connecting to a load of impedance Z_L as shown in Fig 4

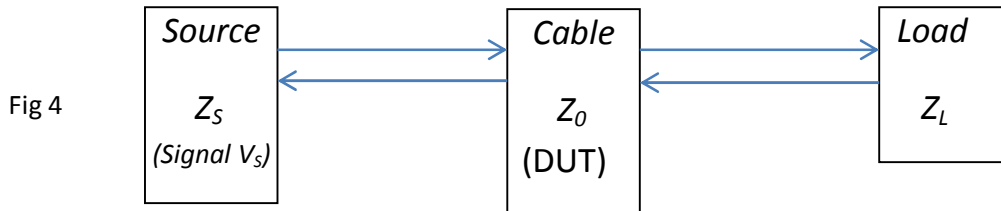Calculate the reflection and reflection coefficient that the cable impedance Z_0 introduces into the circuit.



The right pointing arrows represent signal transmission from source to load, and the left pointing arrows represent the reflected signal.

Hint: Consider carefully the Voltage and Currents at each element and use the definition of Γ

Reflection co-efficient: -

(use blank sheet - page 6 for calculations)

/2

Setup an experiment that looks logically equivalent to the one in Fig 4.

The source is a function generator set to square wave at 1 MHz, 10% duty cycle (it will become clear why we are using such a high frequency and small duty cycle for this experiment)

> The source impedance Z_S is noted on the front panel of the function generator, take note of it.

> We will use a simple resistive load Z_L of different values in the following measurements.

QB₂: Draw your detailed circuit diagram translating the logic of Fig 4 into an experimental setup.

Note especially the points where you will connect your DSO probe.

Hint: Only one channel of the DSO is needed to perform the measurement: Your objective is to measure the signal and reflection - it is necessary to probe this at only one location in Fig 4. Decide which is the best location considering the fact that you want the source signal and the reflection to be well separated in time so that they can be resolved on the DSO trace.

/1

Name: _____

Roll Number: _____

Part C: Measurement of reflections.

Connect one end of the cable (core + shield) to the function generator. The load Z_L is connected between the core + shield at the other end.

Draw a detailed diagram of the observed DSO trace under the following conditions. Note carefully the time positions of features in the signal traces observed.

Explain each trace based on your calculation of the reflection co-efficient in QB₁ above:

1) $Z_L = \text{Infinite}$ (core + shield left unconnected)

/2

2) $Z_L = 0$ (core + shield short-circuit)

/2

3) $Z_L = 51\Omega$ (resistor of 51Ω connected between core + shield)

/2

What would be your recommendation to a novice designer in choosing the cable impedance Z_0 so as to minimize unwanted reflections?

/0 (Advice is free!)

Name: _____

Roll Number: _____

Part D: Speed of light in coaxial cable

a) Measure the length of the coaxial cable given to you.

In your circuit setup, you will likely see reflections of the square wave propagating back and forth in the cable. Each reflection travels at the effective speed of light in the dielectric medium of the cable. You know the length of cable. Putting the two values together, obtain the speed of light in your co-axial cable. *Note: the speed of light is 3×10^8 m/s in vacuum. It is different depending on the properties and geometry of dielectric medium in the cable you are testing. Cables used for RF signal transmission have standardized dielectric media with specific values of the speed of propagation – these cables are labelled as RG59, RG60, RG62 etc. depending on the desired application speed of signal propagation.*

/2

Further work: Note in particular the DSO trace for the case where $Z_L = \text{infinite}$ i.e. there is an open circuit between the core and shield of the cable. The signal is reflected by the open-circuit load and attenuated by the resistive part of Z_0 . You can measure the time lapse between the signal and its reflection. By testing a known good cable with good termination, you can determine the speed of transmission in the cable. Consider the case when you have an arbitrarily long cable (say 3km between IIT-B power plant and H-12) and there is a break in the cable somewhere due to wildlife attack (aka hungry mice). It is practically difficult to dig up the entire length of cable to determine the location of the break by visual inspection. Using the 'time-domain reflection' technique worked out above, you can determine the location of the open-circuit (or short-circuit) by transmitting an RF signal from the source and observing the time it takes for reflections to arrive back.

Part E: Test a broken cable

We purchased one spool of 90ft (27 m) red twin co-axial cable from Lamington Road. It is still wrapped in a spool. Simple electrical continuity test (resistance measurement) indicates that there is damage (open-circuit/short-circuit) somewhere along the length of the cable. By using the techniques developed above, determine:

- a) Location in meters from one end of the cable where it is damaged
- b) Nature of the damage – is it open circuit or short-circuit between the core and shield?

/2
Bonus

Name: _____ *Roll Number:* _____

Space for calculations: