

Name: \_\_\_\_\_

Roll Number: \_\_\_\_\_

## Laboratory 8


A:	/5B:	/4C:	/6 Tot:	/15
----	------	------	---------	-----

### Relaxation Oscillators

This lab consists of three modules. We will see how parasitic effects can occasionally be used to a designer's advantage

#### Part A: Capacitor connected at Input

Fig 1:  $C_s$  at source

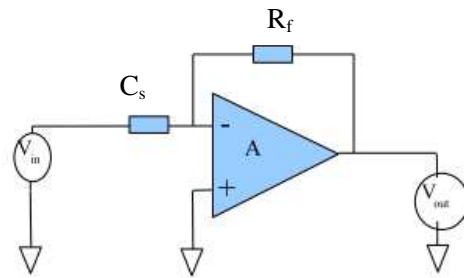

Consider the circuit of Fig 1. Notice the difference from standard inverting feedback amplifier: the *source* resistor has been replaced by a capacitor  $C_s$ .

**Q1:** Calculate the *time-domain* response of  $V_{out}$  to  $V_{in}$  as in Part A. The time-domain response requires you to apply the golden rules of opamp design *and* the current-voltage relationship for a capacitor  $I = C \frac{dV}{dt}$  followed by some algebra.

Current at (-) input :  $V_o/R + C \frac{dV_{in}}{dt} = 0$  so  $V_o = -RC \frac{dV_{in}}{dt} \rightarrow$  Differentiator (with - sign)

/2

**Q2:** Choose suitable values of the passive components  $R_s, C_f$  such that the time constant of your design is 1 ms.

/1

**Q3:** Build the circuit of Fig 2 and drive it with a *square*  $V_{in}$  of amplitude 2V peak-to-peak. Note that  $C_s$  is in the signal path, so the type of capacitor used is important. Choose wisely! Draw a diagram of your observations here and verify that your calculations of Q1 above are correct.

Square differentiate  $\rightarrow$  flat 0 *except* +/- delta functions at edges

Delta function  $\rightarrow$  opamp output saturates and rings after it comes out of saturation.

Can fix this by adding  $R_f/2$  in series with  $C_s$  to set a very low gain.

/2

Name: \_\_\_\_\_ Roll Number: \_\_\_\_\_

**Part B: Comparator**

Recall the simple comparator (with hysteresis) circuit using positive feedback we studied earlier in Lab 2. The function of a comparator is to feedback a fraction of  $V_{out}$  to the (+) input so that when  $V_{in}$  exceeds a threshold set by the feedback fraction  $R_f^+/R^+$ , the output switches to  $-V_{sat}$  and when  $V_{in}$  falls below threshold, output switches to  $+V_{sat}$ .

Use your memory/logic and draw the diagram of a simple comparator circuit here. Set the reference voltage for comparison to  $V_{sat} * (R^+/R_f^+ + R^+)$ .

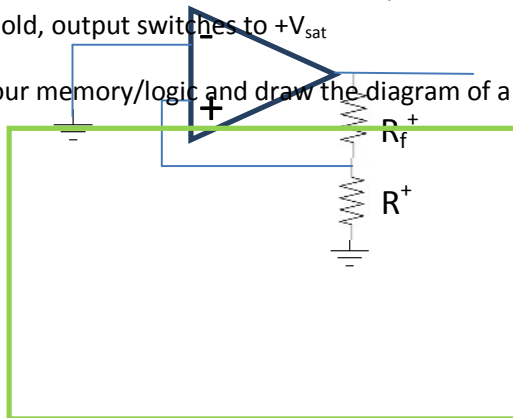


Fig 2: Simple comparator with positive feedback. Set the reference voltage for comparison to  $V_{sat} * (R^+/R_f^+ + R^+)$

/1

/0.5

**Q1:** For  $V_{in} = 0$ , predict the values of  $V_{out}$  in your circuit:

a) What is  $V_{out}$  at  $t=0$  immediately when the circuit is turned on?

0V

/0.5

b) For an *ideal* power supply that turns on  $\pm V_{cc}$  as a step function, what is  $V_{out}$  in the very short time  $\sim$  microseconds after the circuit is turned on?

Rises to  $+$  or  $- V_{sat}$  limited by the slew rate  $\sim 0.1/\mu s$  : so it will take  $\sim 10 \mu s$  to reach  $V_{sat}$

/0.5

c) What is  $V_{out}$  in steady state after the circuit has been on for a few seconds:

+/-  $V_{sat}$ 

/0.5

d) What determines the steady state value of  $V_{out}$  in question c) ?

Sign of input offset voltage  $V_{os}$

**Q2:** Connect up the circuit you have designed in Fig 2 and *demonstrate* the validity of your predictions. Use this space to record your DSO observations of  $V_{out}$  in detail.

**Note that  $V_{in} = 0$  for a), b), c)**

Your observations for (b) may differ from prediction because the power supply is *not* ideal. Observe the voltage  $\pm V_{cc}$  supplied by the power supply to the circuit at  $t=0$  on the DSO to validate your prediction.

Name: \_\_\_\_\_ Roll Number: \_\_\_\_\_

**Part C: Relaxation oscillator**

Use your observations and conclusions from Parts A and B to make a circuit with one opamp that demonstrates the following behavior:

1. It's  $V_{out}$  oscillates between two fixed values (for example  $+V_{sat}$  and  $-V_{sat}$ )
2. It has no external  $V_{in}$  applied
3. The oscillation time period is 1 ms

*Hint: You will need to combine the concepts of Parts A and B*

Draw your circuit design here. Calculate and mark the value of the components required.

Comparator with differentiator in negative feedback loop

Relies on delta function created by 0 to  $+V_{sat}$  switching to force output to switch to  $-V_{sat}$  and vice-versa

/2.5

/3.5

This type of oscillator is called a 'Relaxation Oscillator'. Build your circuit and demonstrate its operation

/2