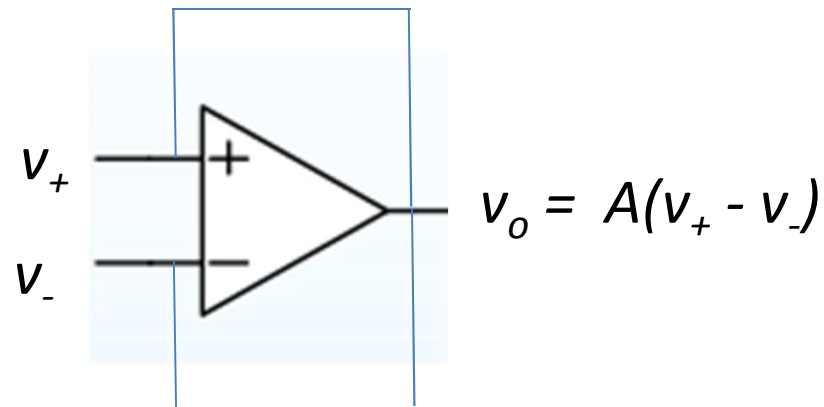


Lecture 2

Positive Feedback Schmitt trigger



Recall simple comparator (Lab 1)

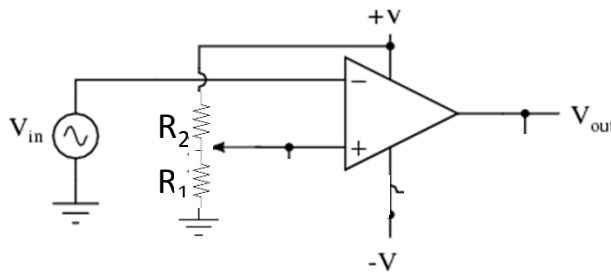


Fig 2: Simple comparator: R_1 R_2 set the threshold voltage for switching v_{out} between $+V_{max}$ and $-V_{max}$


what is v_+ ?:
$$v_+ = \frac{R_1}{R_1 + R_2} V \equiv V_T$$

$$v_- = v_{in}$$

For $v_{in} < V_T \rightarrow V_{out} = +V_{max}$

For $v_{in} > V_T \rightarrow V_{out} = -V_{max}$

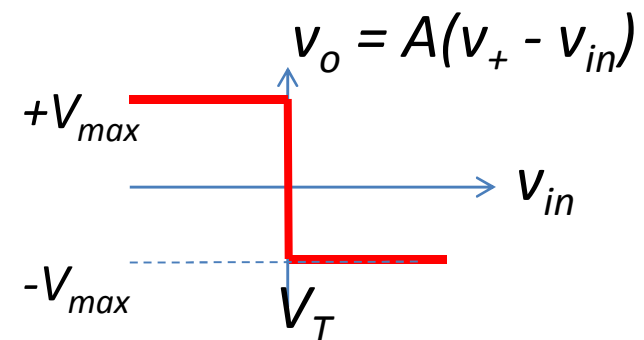But for noisy v_{in} close to V_T ,
 V_{out} swings crazily between $+V_{max}$ & $-V_{max}$



Review of Lab 2

POSITIVE feedback is good


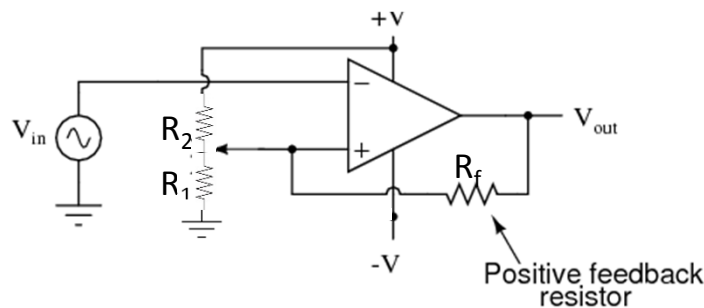
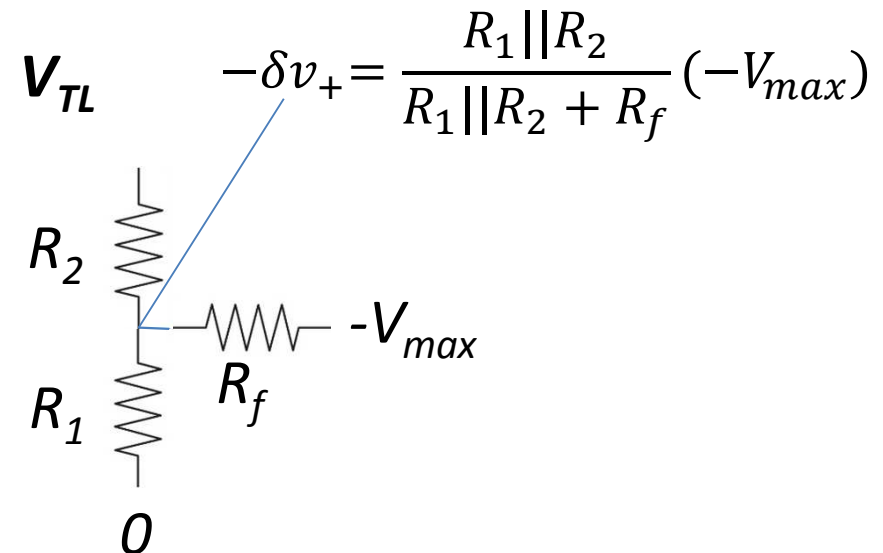


Fig 3: Positive feedback through R_f stabilizes the circuit response

$$v_+ = f(v_{out}, R_1, R_2, R_f)$$


v_{out} has two values: $+V_{max}$, $-V_{max}$

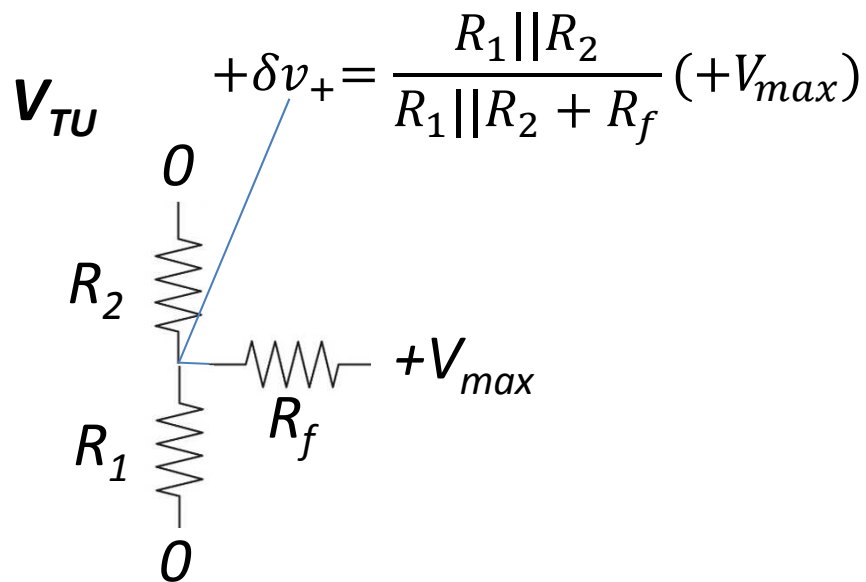Apply superposition: V_T already set by R_1, R_2 . R_f sets $+\delta v_+$ and $-\delta v_+$



Set independent sources to zero $V, v_{in} \rightarrow 0$


Threshold splits in two

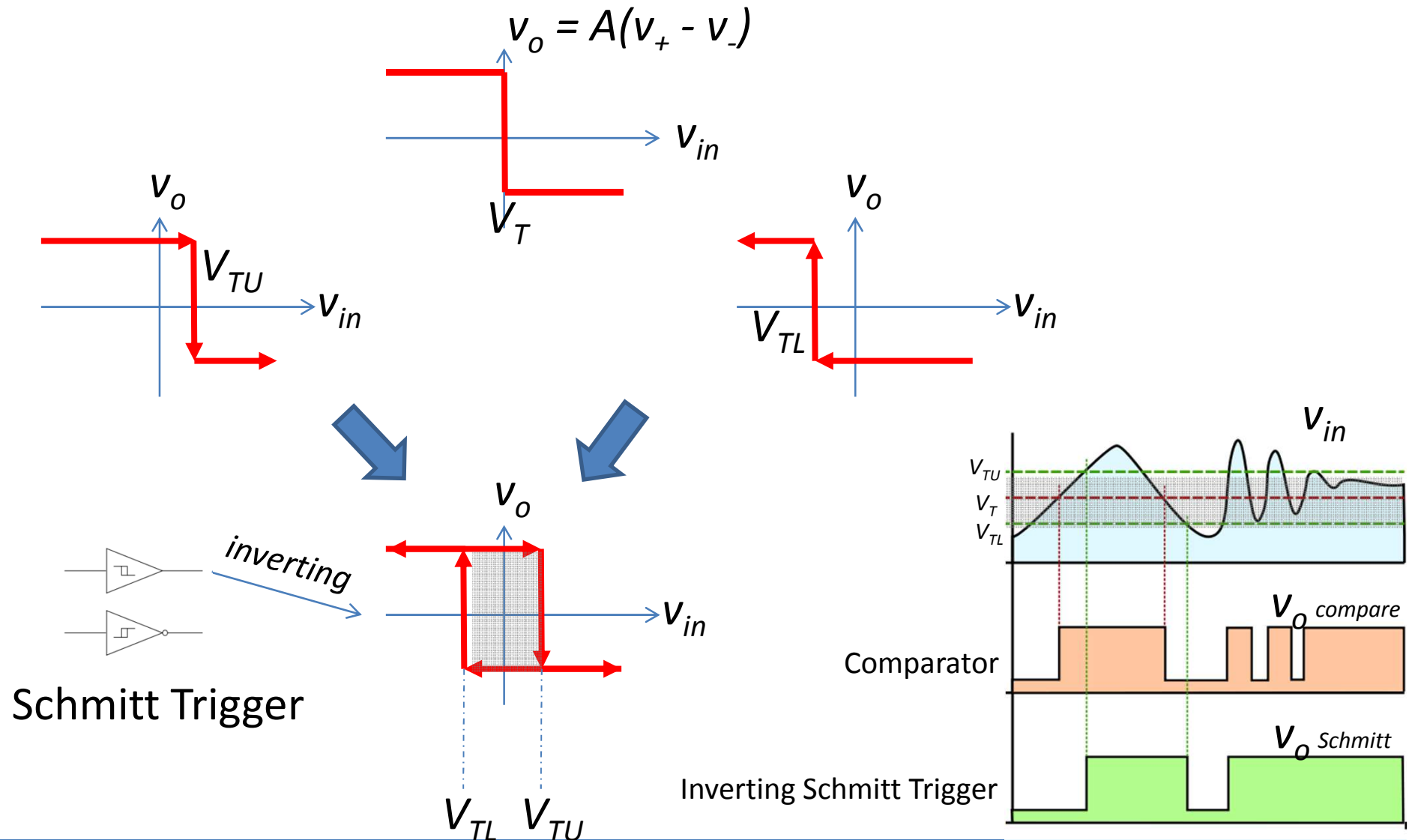

Summary

In a figurative sense...

Simple comparator

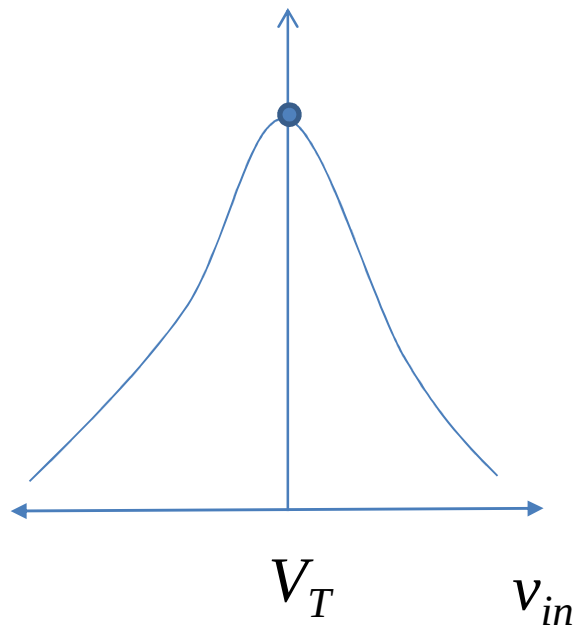

Schmitt trigger
(positive feedback)

