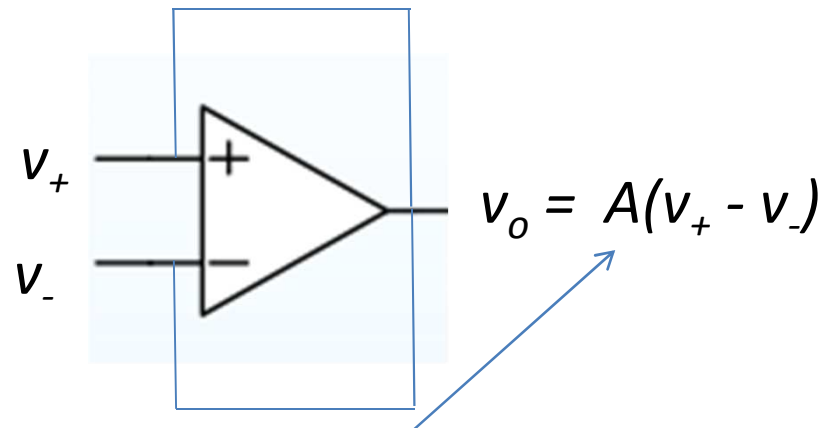


Lecture 3

Negative Feedback



Open Loop: $A \sim 10^5$ almost never used

NEGATIVE feedback is BETTER than POSITIVE feedback


Consider a Heater control System:

When the temperature falls, the heater turns on

When the temperature rises, the heater turns off

Let v_{in} represent input from a thermometer

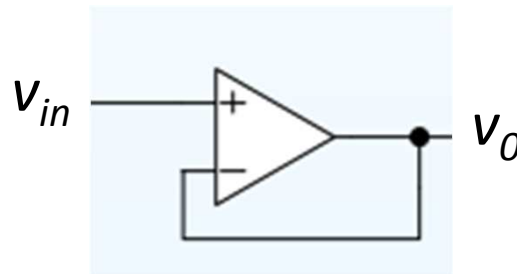v_o represent the control signal to the heater: v_o high $\rightarrow$ heater on



When it's cold, v_{in} falls $\rightarrow v_o$ falls $\rightarrow v_-$ decreases $\rightarrow (v_+ - v_-)$ increases $\rightarrow v_o = A(v_+ - v_-)$ will tend to rise i.e. heater turns on.


NEGATIVE feedback: something happens $\rightarrow$ the system tries counteract it

Simple Negative feedback

Consider a Heater control System:

When the temperature falls, the heater turns on

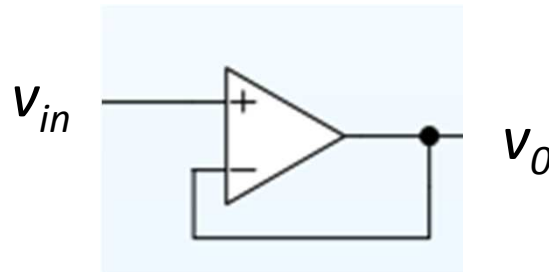When the temperature rises, the heater turns off



$$v_o = A(v_+ - v_-)$$

$$v_o = A(v_{in} - v_o)$$

$$v_o (1+A) = A v_{in}$$


$$v_o = \frac{1}{1 + 1/A} v_{in} \rightarrow v_o = v_{in}$$

A large

In steady state, v_o tracks v_{in}

Negative feedback makes inputs equal

v_+ and v_- are equal – how and why ?

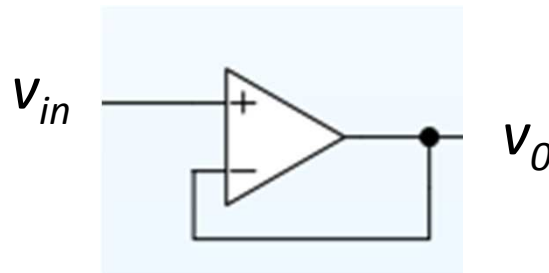

$$v_o = A(v_+ - v_-)$$

$$v_+ - v_- = \frac{1}{A} v_o \rightarrow v_- \sim v_+$$

Output does whatever it can to make the inputs equal

Golden Rules of Negative Feedback

1. Output does whatever it can to make inputs equal
 v_- is 'slave' to v_+ in negative feedback
2. Inputs draw no current

Summary

Today:

- Negative feedback
- Golden Rules I and II of negative feedback