

Lecture 5

Opamp imperfections


Reference:

Analog Devices, Opamp basics tutorial:


<http://www.analog.com/static/imported-files/tutorials/MT-038.pdf>

Consider opamp internals

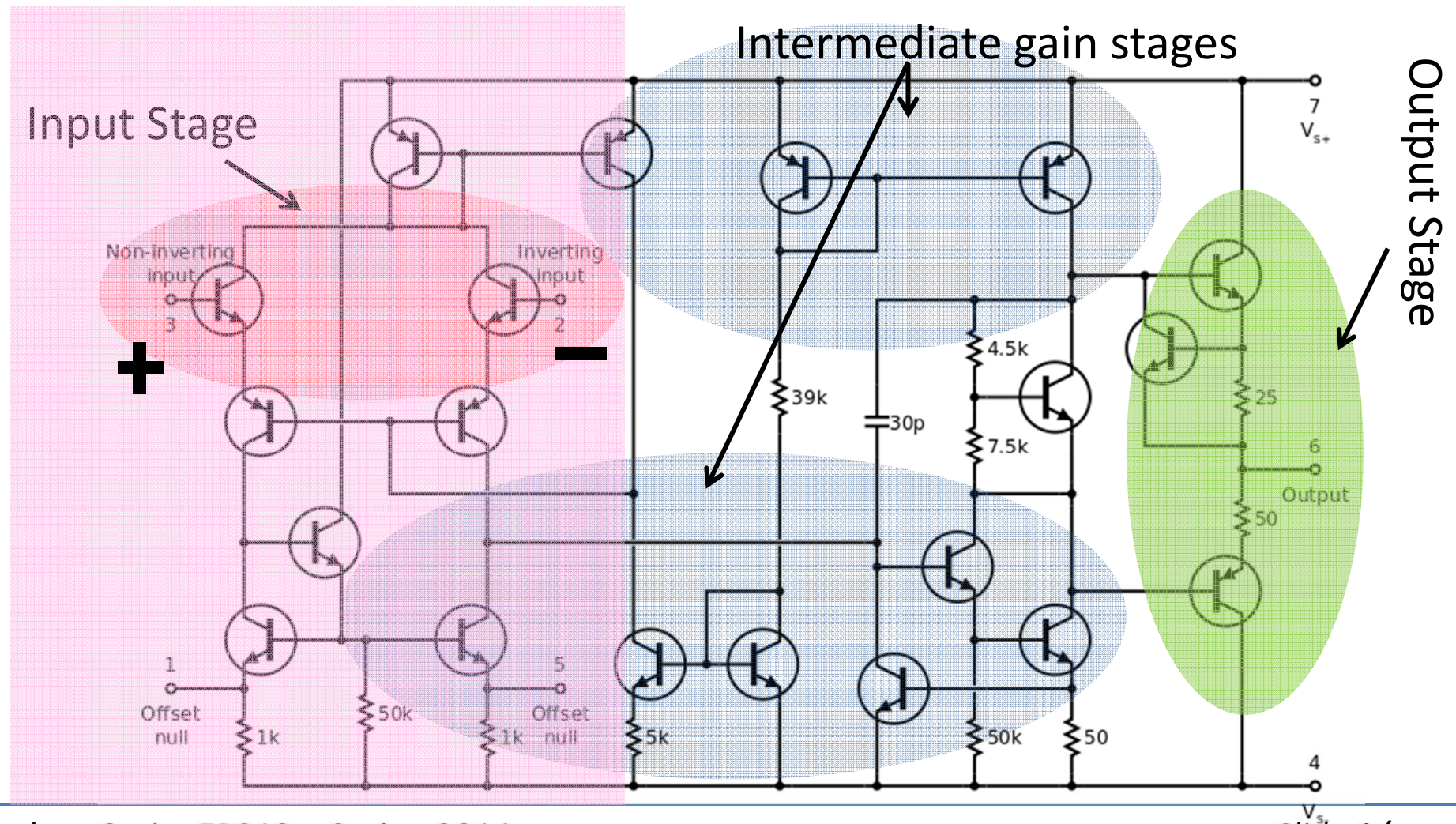OpAmp integrates precision matched actives+passives in one IC




Simplified input stage

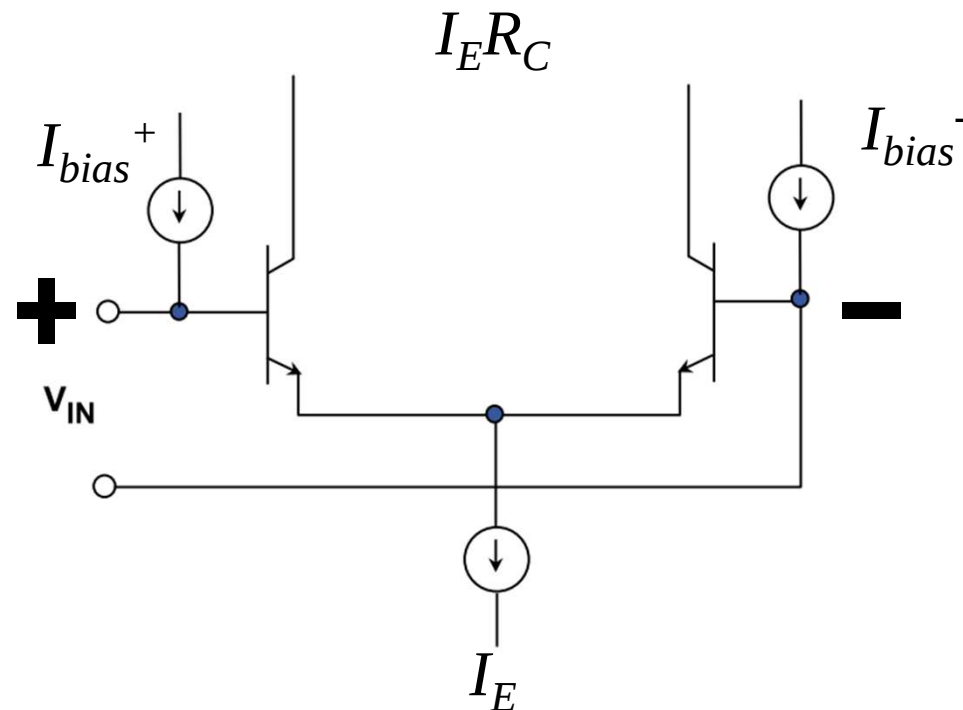


Imperfection 1: V_{os}

Input offset voltage V_{os}

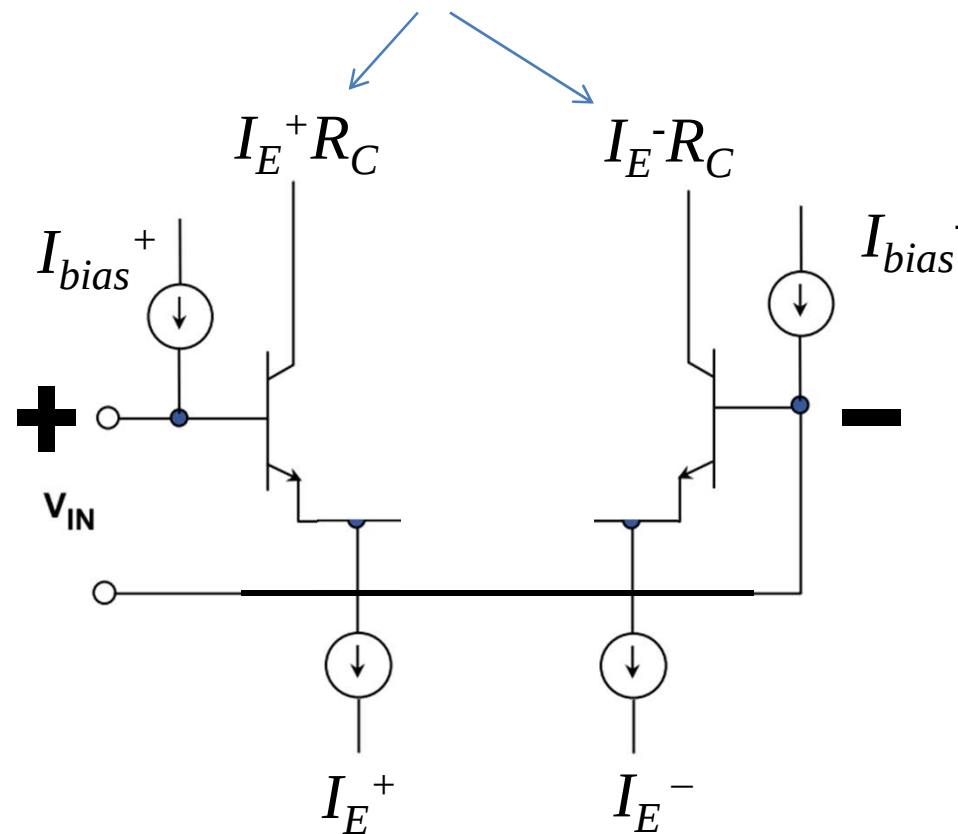
If I_E^+ and I_E^- are different, voltages at the collector terminals will be different



You can compensate V_{os}

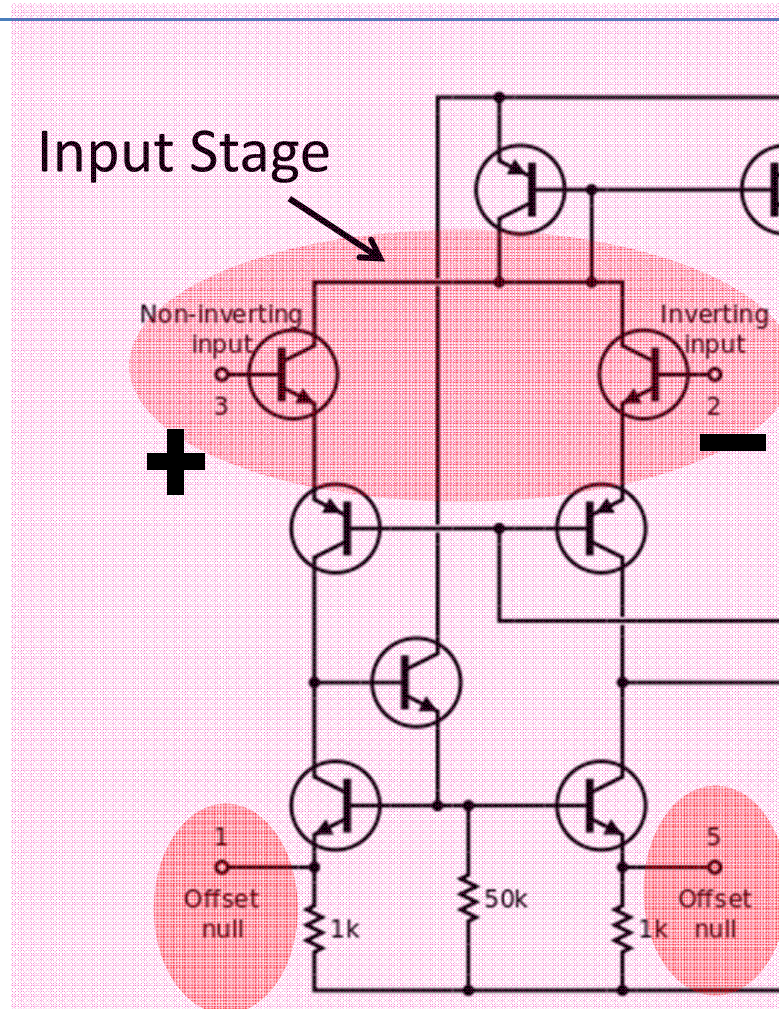


Adjust I_E^+ & I_E^-

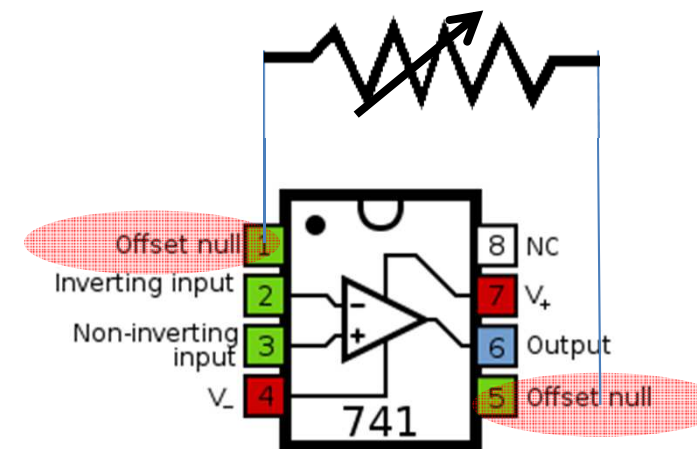

Imperfection 2: I_{bias}


$$I_{bias}^+ \neq I_{bias}^-$$

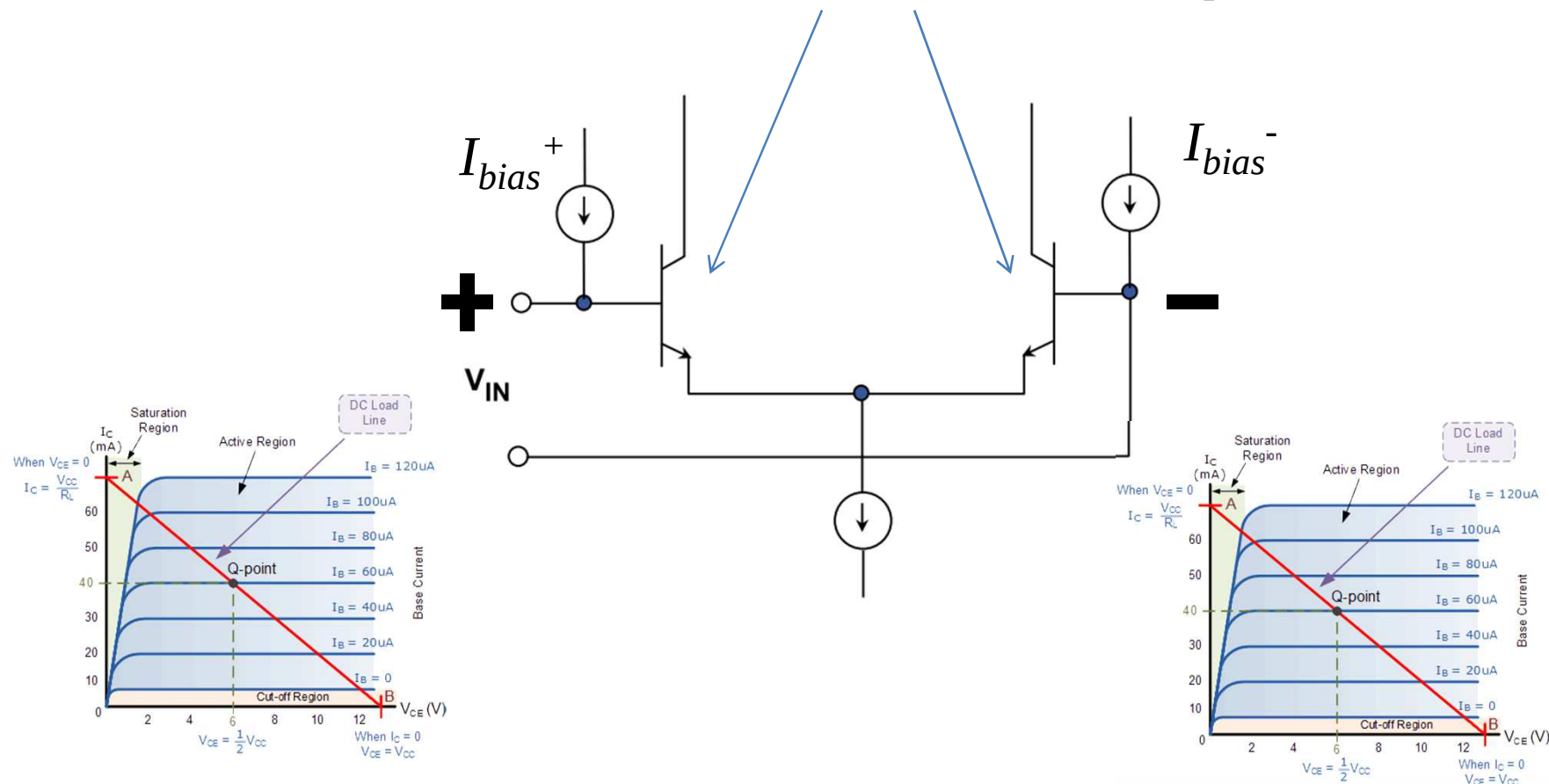Sets the two transistors at two different Q points




Cannot compensate for I_{bias}

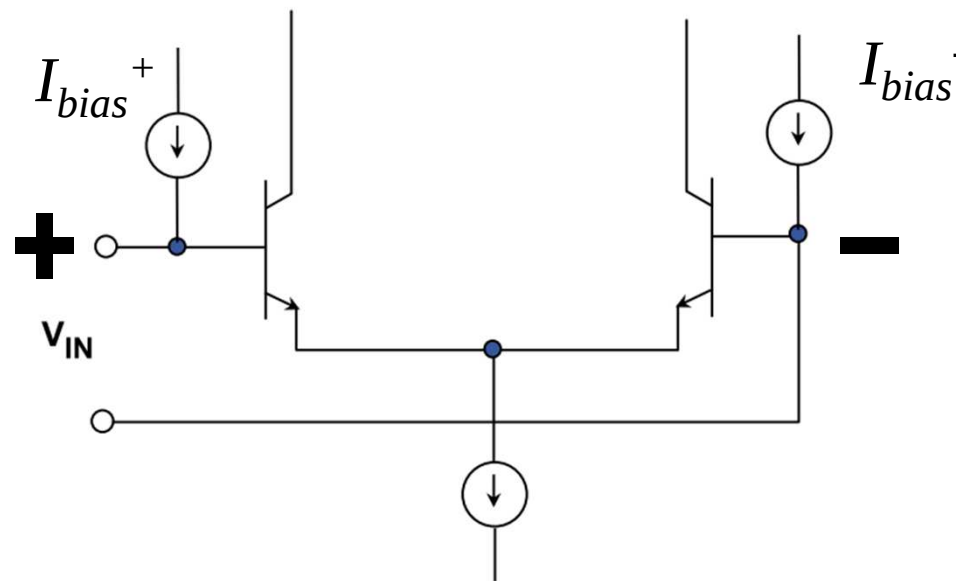Good news: I_{bias} is usually very very small




I_{bias} can be bad in a poor circuit

Bad news: I_{bias} multiplies R_{in}

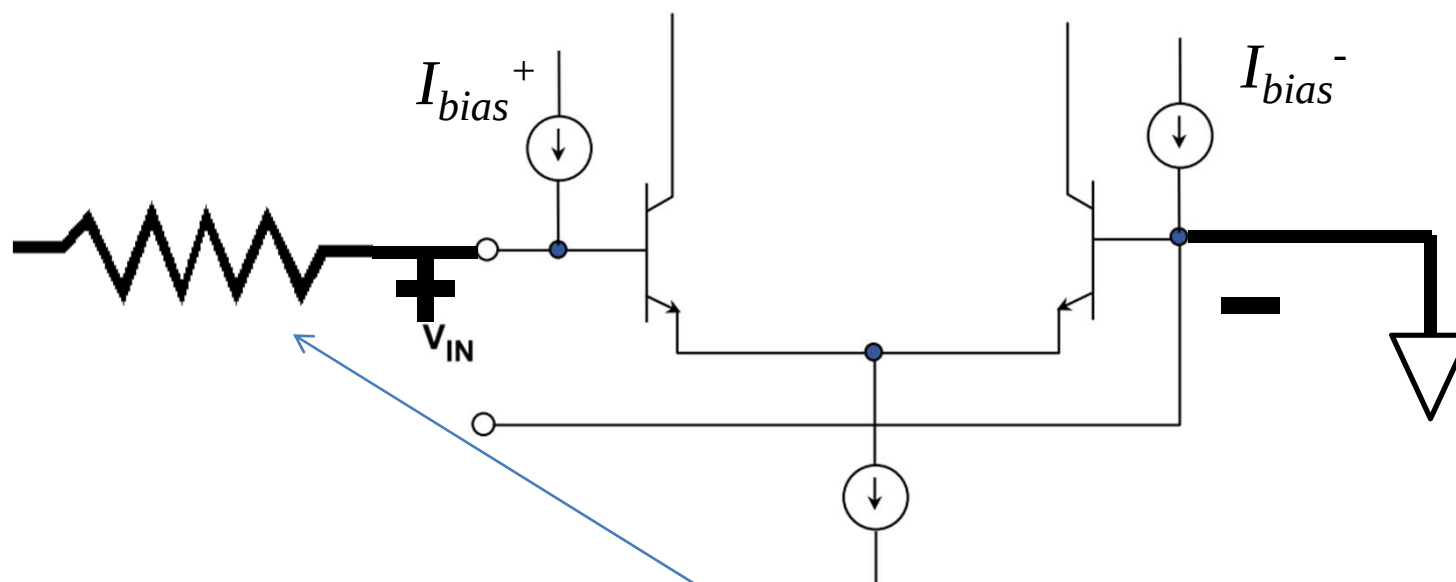


Depending on R_{in} , will cause a *fake* $I_{bias}^+ R_{in}$ appear as v_+ even if $v_{in}=0$

Must 'bias compensate' a circuit

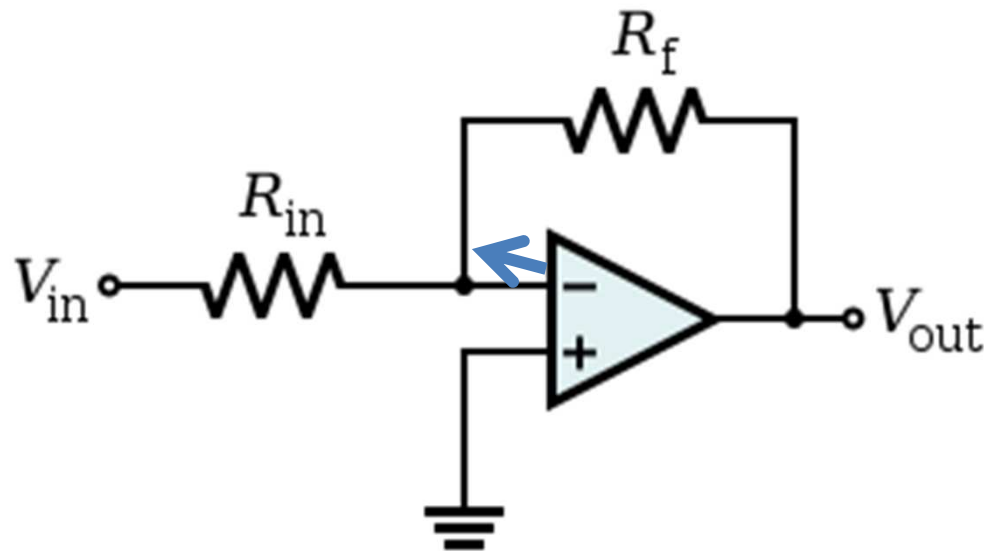

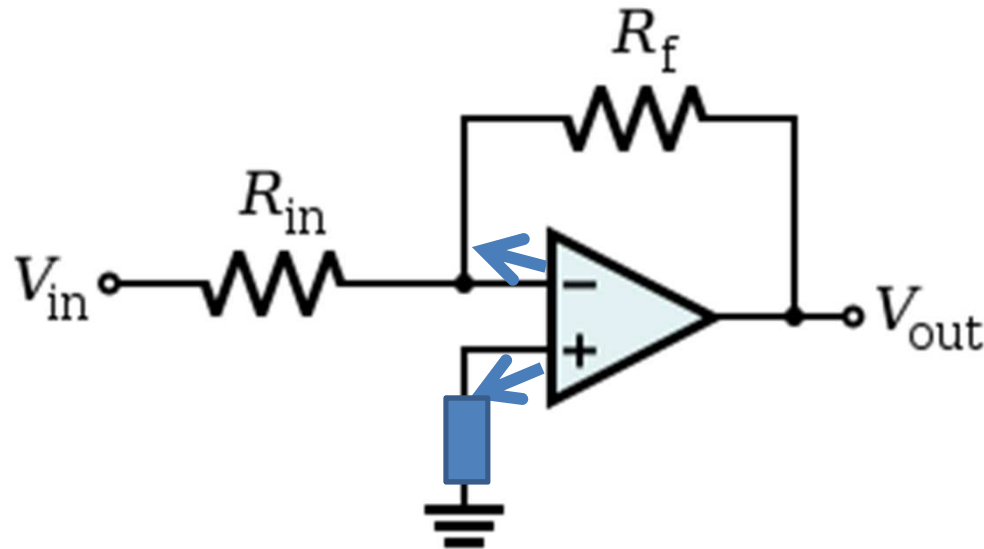1. At DC, with $V_{in} = 0$, what is the effective R 'looking out' from - ?
2. If there is I_{bias}^- , what is effective V_{in} ?
3. If $I_{bias}^+ \approx I_{bias}^-$ what must you do at the + terminal to cancel (2)

Must have equal DC resistance 'looking' out of each input terminal



1. Calculate effective R 'looking' out from '-' terminal
2. Put in equivalent R_{eff} in the other '+' terminal
3. $R_{eff} * I_{bias}^+$ voltage drop cancels $R_{eff} * I_{bias}^-$ at $V_{in} = 0$

Preparation for Lab 5

- Read up on background of V_{os} & I_{bias}
- Techniques for measuring V_{os} & I_{bias}
*not trivial! - measure an intrinsic property of the device
without applying V_{in}*