

Lecture 7

Impedance matching & power transfer

Reference:

“bible” of RF circuit design:


Thomas H. Lee “The design of CMOS Radio-Frequency Integrated Circuits”

What is “Radio Frequency” ?

Any signal with frequency content 20 kHz to ~ 100 GHz


Consider what happens when we introduce L and C into a circuit

Series

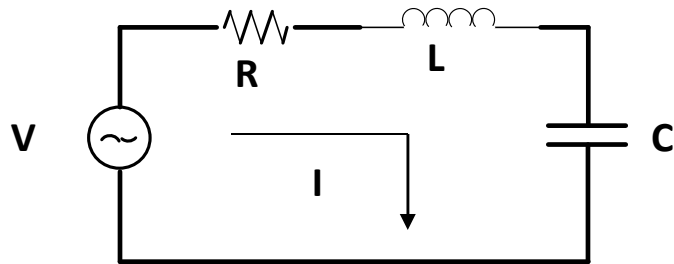

$$V = I \left[R + j\omega L + \frac{1}{j\omega C} \right]$$


Parallel

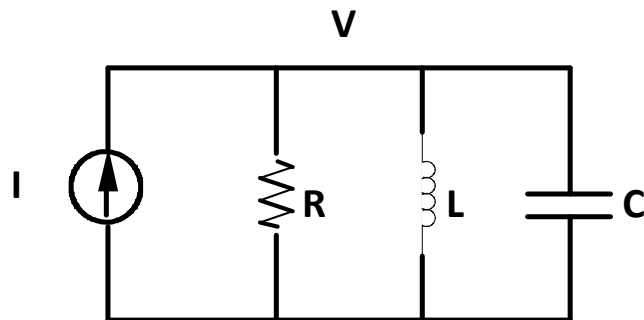

$$I = V \left[\frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right]$$

The resonant circuit 'picks' out a frequency

Series

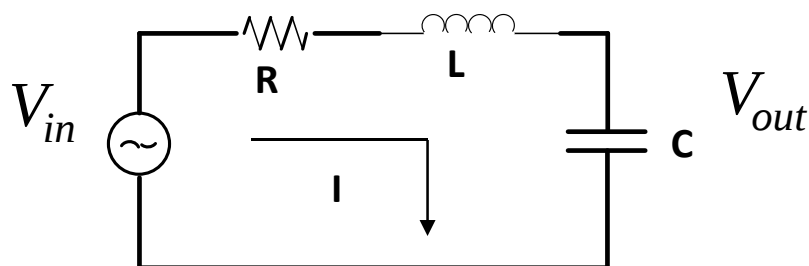

$$V = I \left[R + j\omega L + \frac{1}{j\omega C} \right]$$

Can show:

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{\omega L}{\sqrt{(\omega L)^2 + R^2(1 - \omega^2 LC)^2}}$$

For $\omega_0 = 1/\sqrt{LC}$: $V_{\text{out}}/V_{\text{in}} = 1$ else < 1

A square wave is really a sum of sines (from Fourier analysis)


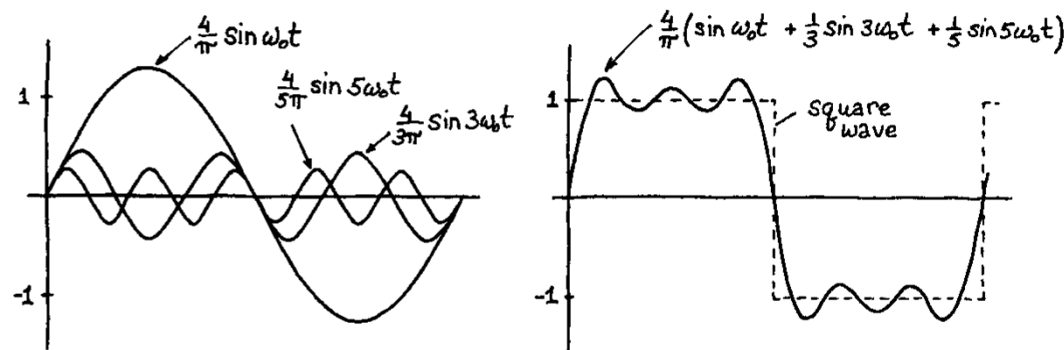



Figure L3.2: Fourier series for square wave

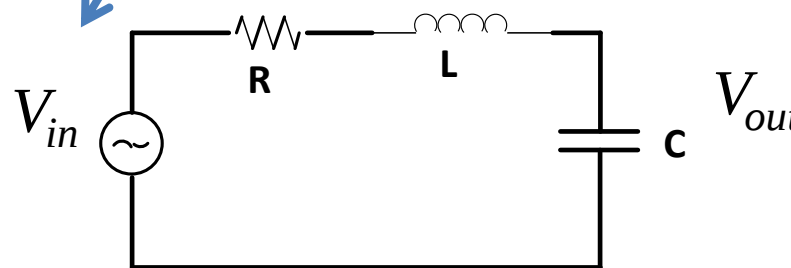When the square wave is applied as V_{in}




Frequencies
near ω_0 will
pass through,
others will be
attenuated

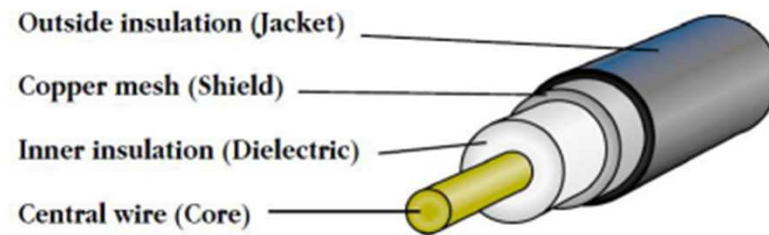
A coaxial cable is modelled as a series LC network



Lossless transmission model

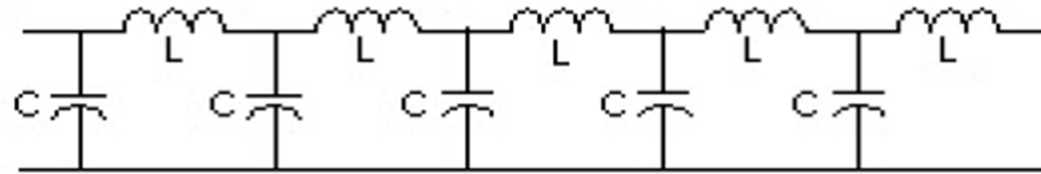


Lossy transmission model

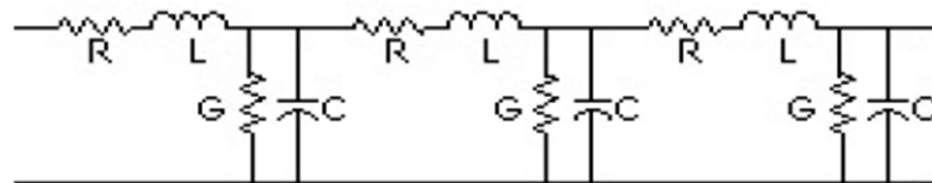

See <http://goo.gl/l3p7s7> for a detailed analysis of a how a cable 'works'

Preparation for Lab 7

Study Cables

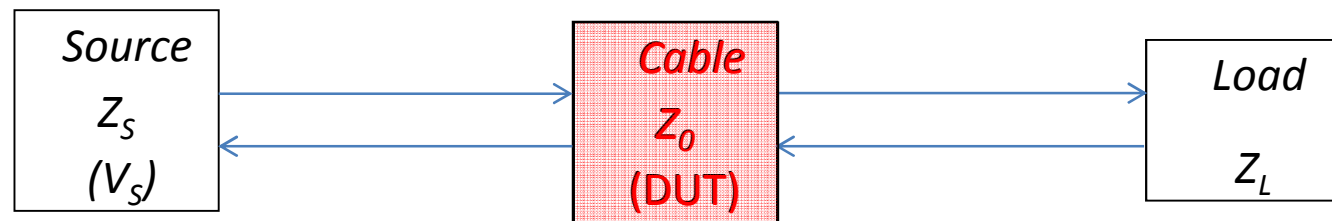

Device Under Test