

# Laboratory Assignment 3 : I/V characteristics

Suggested reading and connection time: 20 min.

## Goal:

In this assignment we will learn a useful technique to *characterize* an electronic part, i.e. obtain it's I/V characteristics. We will use some of the more advanced features of a DSO to make such possibly tedious measurements easier. No graph papers will be used.

You have already learnt the basic operation of a Function Generator and Digital Storage Oscilloscope in Lab 2.

In this lab, we will use the *differential* voltage signal provided by the function generator on a red cable connected from its back panel. This cable has three connectors – the red and white present a differential voltage which swings between  $+V$  and  $-V$  and the green connector presents the halfway point: it is always at  $(+V-V)/2 = 0$ . Note that this 0V is not related to the 'earth-ground' potential.

For this entire experiment, connect a circuit in the configuration shown in Fig 1.

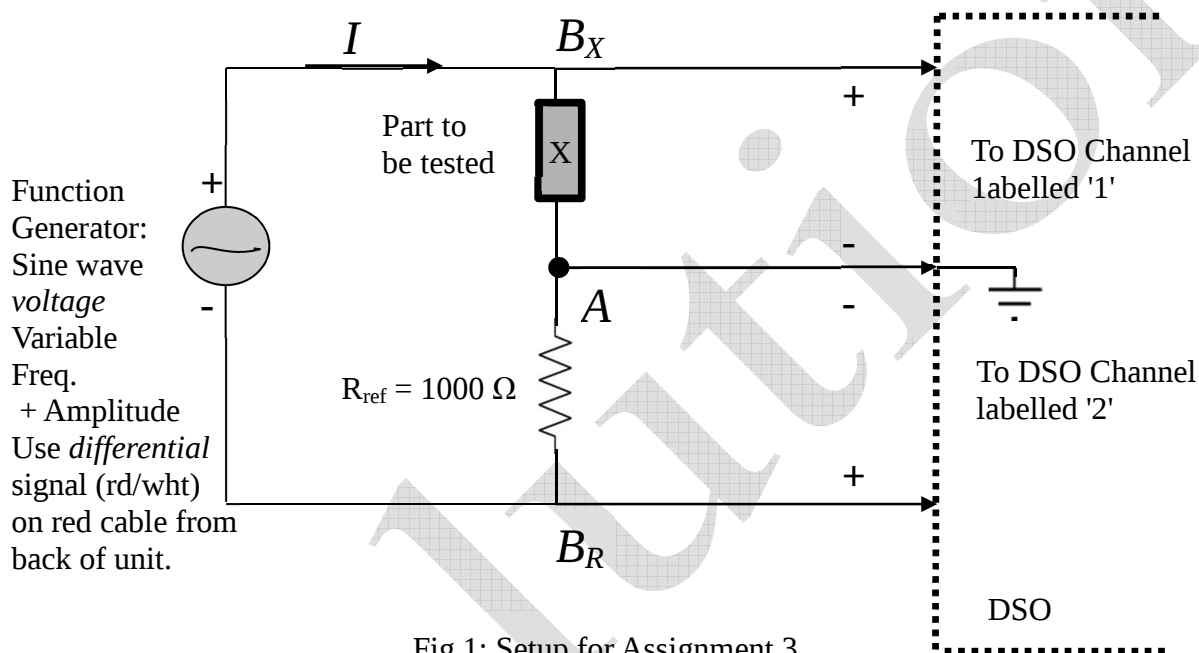


Fig 1: Setup for Assignment 3

Here are a few things you should notice when making the connections:

- ⤴ The function generator is producing a *differential voltage* signal swinging between  $+V$  and  $-V$ : (the amplitude is set by the knob on the front panel). The green wire is not used for this setup.
- ⤴ On the DSO both channels have their negative terminals (the outer shields of the BNC connector) internally connected to earth ground for safety.
- ⤴ You must learn to keep track of this distinction between a differential (+/-) signal, and a signal whose negative terminal is fixed at ground potential (a single-ended signal). It is very important in analog electronics – we will use it many times during the semester.
- ⤴ The number of connections to be made in the above circuit is very small: however, you must make sure that the connections are secure. A loose wire can inject a lot of noise into your measurement and lead you off into completely wrong conclusions

Note: The following experiments *must* be performed in the suggested times. So make doubly sure that your connections are secure before putting in the part X to be characterized.

**Part 1: The Diode***Suggested times: Part A: 40 min, Part B: 30 min*

Put in a diode as Part X in Fig 1. Use input signal frequency of 100 Hz.

**Part A)** By adjusting the various controls on the DSO, obtain the I/V characteristics of the diode. Normally, the DSO plots the signals measured on channels 1 and 2. However, it can be put into a mode which plots channel 1 v/s 2 (it's called X-Y mode). Determine which control button does this.


Observe and note the following:

1. From the markings on the DSO probe, what is the input resistance seen by the points ( $B_X-A$ ) i.e. device X and ( $B_R-A$ ) i.e.  $R_{ref}$  looking into the DSO?        $\sim 1\text{ M}\Omega \parallel \text{pF}$
2. Based (1), what is the path of current  $I$  at the junction A?       through X and  $R_{ref}$  (no I into DSO)
3. Accordingly, what does channel 1 measure?        $V_X$
4. What does channel 2 measure?        $V_{Rref}$

Using Ohm's law and the above information, assuming  $R_{ref}$  is a perfect resistor, one axis of the X-Y measurement plot can be simply converted into a different quantity

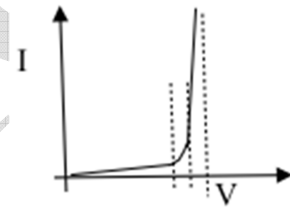5. What is this quantity?        $I_X$

Based on the answers to all the above questions, draw a plot of the measured I-V characteristic of the diode here:



*Hint: Consider carefully the voltage polarities applied to Part X and  $R_{ref}$  with respect to the junction point A : you may need to invert one of the channels to get a sensible V/V graph. You can go into the Channel menus of the DSO to invert the signal.*

6. What is the voltage at which the diode just starts conducting? \_\_\_\_\_
7. What is the voltage at which the diode reaches full conduction? \_\_\_\_\_

**Part B)** Keeping the above setup same, change the input function generator signal to a high frequency: Redraw the new observed I-V characteristics here, and state a hypothesis to explain your observations

i) For frequency = 1 kHz

ii) For frequency = 10 kHz

At  $\sim 1$  kHz hysteresis is seen in forward bias      At 10 kHz, in reverse bias too, the diode current is  $>0$   
 Diode's depletion zone width acts as an effective capacitor in parallel. When voltage changes, the capacitor has a finite time constant to discharge and remove stored charge in the depletion layer.

Answer: At high frequency, heat dissipation in the diode (which appears like an equivalent series resistor) and *capacitive* effects, cause the observed characteristic to become non-linear. The diode has a certain delay time in going from forward to reverse bias. At high frequency, the common diode used in our lab cannot switch fast enough, and acts like a capacitor in the lower left part of the characteristic. It never really 'turns off'. So the characteristic looks somewhat like an apostrophe ' For applications where high frequency switching of diodes is important, special diodes called Schottky diodes are typically used.

Note: you will have to magnify the scale and examine the traces around the origin to notice peculiarities.

*Hint: Normally, diodes are specified to operate at AC line voltage (60 Hz) as rectifiers. For high frequency operation, a different type of diode, called a 'Fast Recovery' diode must be used.*

**Part 2: The Resistor** *Suggested times: Part A: 20 min, Part B: 30 min, Part C: 30 min*

Put in a resistor of *unknown* value  $R_{unknown}$  in place of Part X in Fig 1.

**Part A)** (You are not allowed to use a DMM!)

**Q.1)** Repeat the technique developed for Part 1A to obtain the I-V characteristic of the resistor. At first try a sine wave input of  $\sim 2V$  amplitude at frequency  $\sim 200Hz$ .  
This should let you make a straightforward measurement.  
Draw your observed I-V characteristic here, making careful note of the slope:

Linear I-V trace: slope gives  $R_{unknown}$

Based on your observations, determine  $R_{unknown} =$  \_\_\_\_\_

**Part B)** Keeping the amplitude low, increase the frequency of the input signal up to  $\sim 10\text{ kHz}$   
Redraw the observed I-V characteristic:

Curve becomes non-linear above  $\sim 5 - 10\text{ kHz}$  : an effect of the parasitic parallel capacitance and series inductive wire connections depending on how the connections have been made. See Lecture notes for details.

**Q.2)** If the observation is different from Part A, state a hypothesis that accounts for the difference:

Bare minimum acceptable hypothesis: each resistor can be modeled as  $(R + 1/j\omega C + j\omega L)$ . In this measurement, at high frequencies the complex term is non-negligible and different for the two devices.  $(R_X + 1/j\omega C_X + j\omega L_X)$  and  $(R_{ref} + 1/j\omega C_{ref} + L_{ref})$ . This causes the elliptical 'Lissajous' type curve observation.

In principle, from the observed major and minor axes of the ellipse,  $L_X$  and  $L_{ref}$  can be derived.

**Observations made by PSarin in testing the setup with DSO on Aug 16, 2012-08-16 (and during the lab)**

|     |      |     |       |       |       |
|-----|------|-----|-------|-------|-------|
| /6  | /2+2 | /3  | /1    | /1    | /15   |
| 1.A | 1.B  | 2.A | 2.B.1 | 2.B.2 | Total |

**Diode I-V characteristics:**

- For some mysterious reason, the I/V curve is rotated by  $+90^\circ$ . Couldn't change it to 'textbook' shape by either inverting X or Y or both. Please recheck connections
- Linear characteristic only up to  $\sim 100$  Hz
- Beyond that, diode becomes non-linear. It 'remembers' its ON state even when the bias is reversed. Need different type of diodes (called fast recovery diodes) that don't have such non-linearities

Generally good settings of DSO:

Display  $\rightarrow$  XY mode

$\rightarrow$  Use Dots

$\rightarrow$  Pixel persistence off

Channel 1 (diode) 500 mV and Channel 2 (1k resistor) 1V scale seems to give good resolution to see 0.7V diode turn-on

Play around with connections and waveform inversion to get the characteristic 'right side up' !

**Resistor I-V characteristics:**

- Amplitude of input used was approximately half the maximum from FG
- Must invert one channel to get positive slope R!
- Curve becomes non-linear above  $\sim 5 - 10$  kHz : an effect of the complex impedance (inductive wire connections depending on how the connections have been made + capacitive input impedance of the DSO) Can see the lissajous type non-linear curve change shape by merely pressing down on Part X.  
Group 1 worked out the detailed mathematical shape of the curve using impedances X and Y – showing elliptical/circular form depending on the resistance values.
- Joule heating effect (Part C below) is very difficult to observe and interpret, hence dropped.  
At large voltage amplitude best seen at very low frequencies  $\sim 0.5 - 1$  Hz  
The trace can be seen in detail moving up and down across quadrants 1 and 3: the slope is equal to the  $R_X$  value near the origin, but becomes sharply higher at the extremes

**Part B)** Increase the amplitude of the function generator to maximum and reduce frequency to 1 Hz. Redraw the observed I-V characteristic:

Joule heating can be seen by zooming into the trace in quadrants 1 and 3: near origin  $R_X$  should be same as in Part A, at the extremes, slope (i.e.  $R_X$ ) increases. Results vary according to the time taken to perform the experiment

Based on this new observation, deduce the value of  $R_{\text{unknown}} = \underline{\hspace{2cm}}$   
If it is different from Part A, state a hypothesis that accounts for the difference: