

# EP215

## Electronics Lab 1


### **Lecture 3**

#### Review of Lab 2


#### Simplest Active device: DIODE

# Review of Lab 2


1. One Diode (voltage) clamp

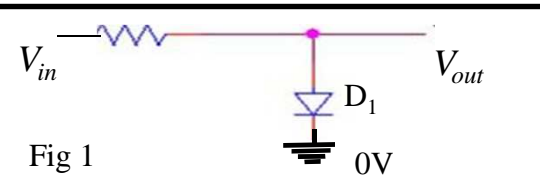


2. Two Diode (voltage) limiter

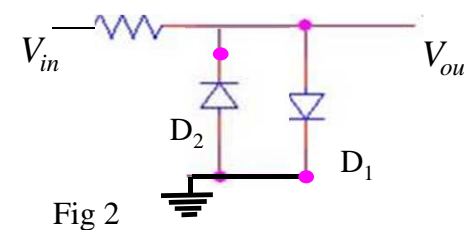



3. One Diode half-wave rectifier

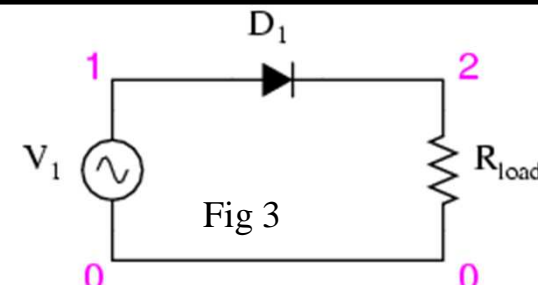

4. Four diode full-wave rectifier

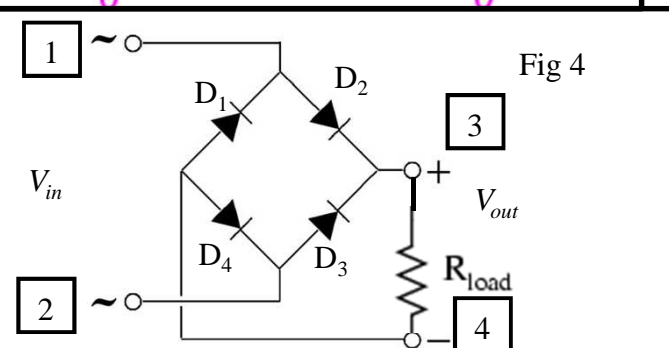

# What happens in a diode clamp?

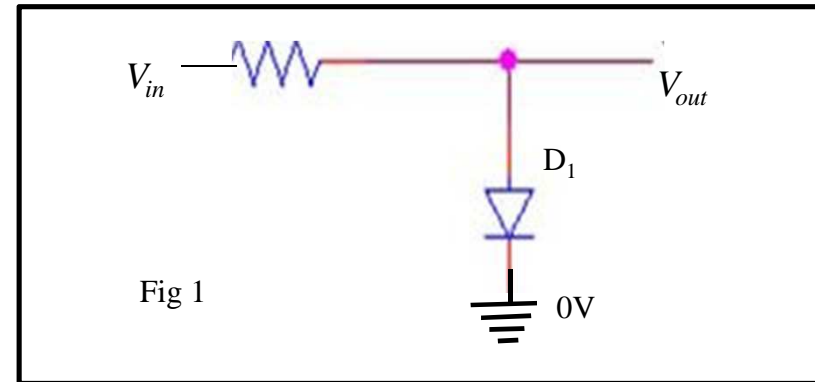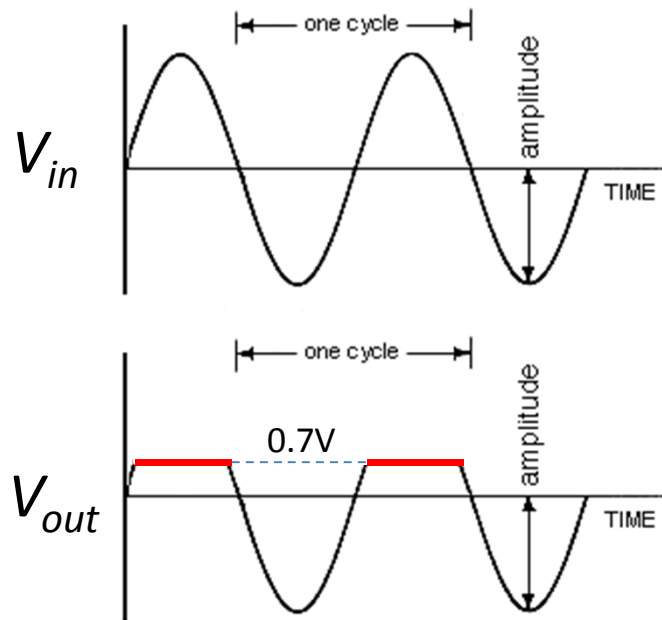

If  $V_{in} < 0.7V$ ,  $V_{out} = V_{in}$

If  $V_{in} > 0.7V$ ,  $V_{out} = 0.7V$



Follow up questions:

1. This circuit only clamps the positive part of  $V_{in}$

What modification would cause it to clamp the negative part of  $V_{in}$ ?

2. What modification would make it clamp both positive and negative ?

# What happens in a diode clamp?

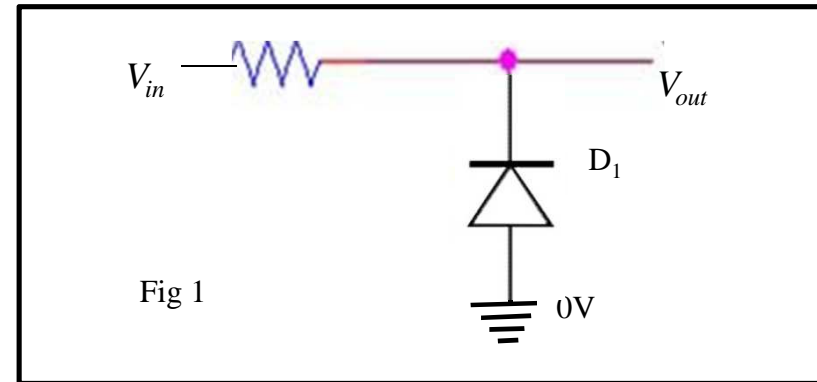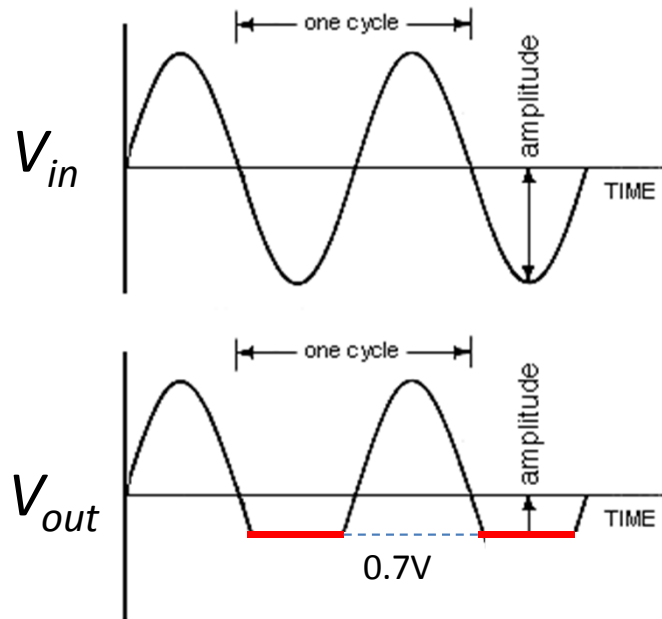

If  $V_{in} > 0.7V$ ,  $V_{out} = V_{in}$

If  $V_{in} < 0.7V$ ,  $V_{out} = 0.7V$

What modification would cause it to clamp the negative part of  $V_{in}$ ?

# Diode Limiter

---

<http://www.falstad.com/circuit/e-diodelimit.html>

# Half wave Rectifier


---

<http://www.falstad.com/circuit/e-rectify.html>
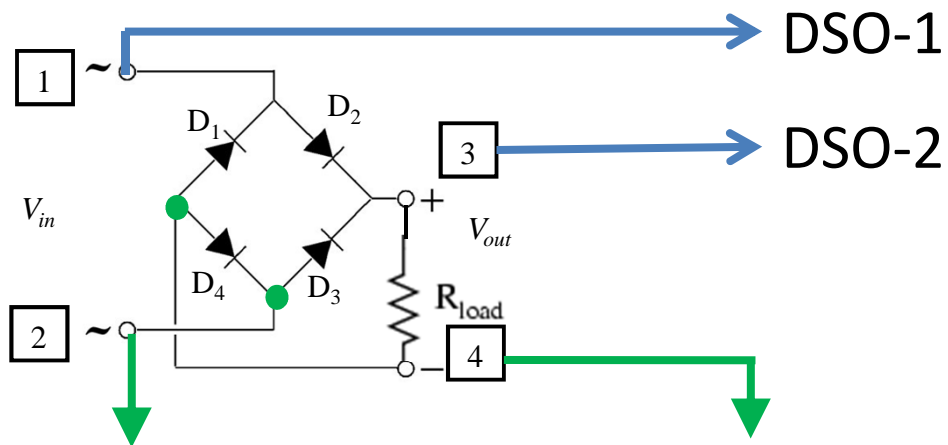
# Full wave rectifier

---

<http://www.falstad.com/circuit/e-fullrect.html>




# Full wave rectifier

---
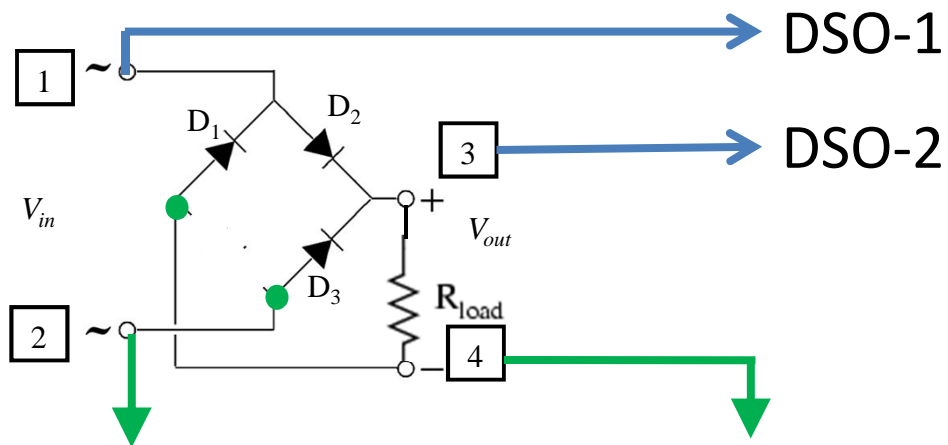
## with measurements of $V_{in}$ $V_{out}$


<http://www.falstad.com/circuit/e-fullrect.html>


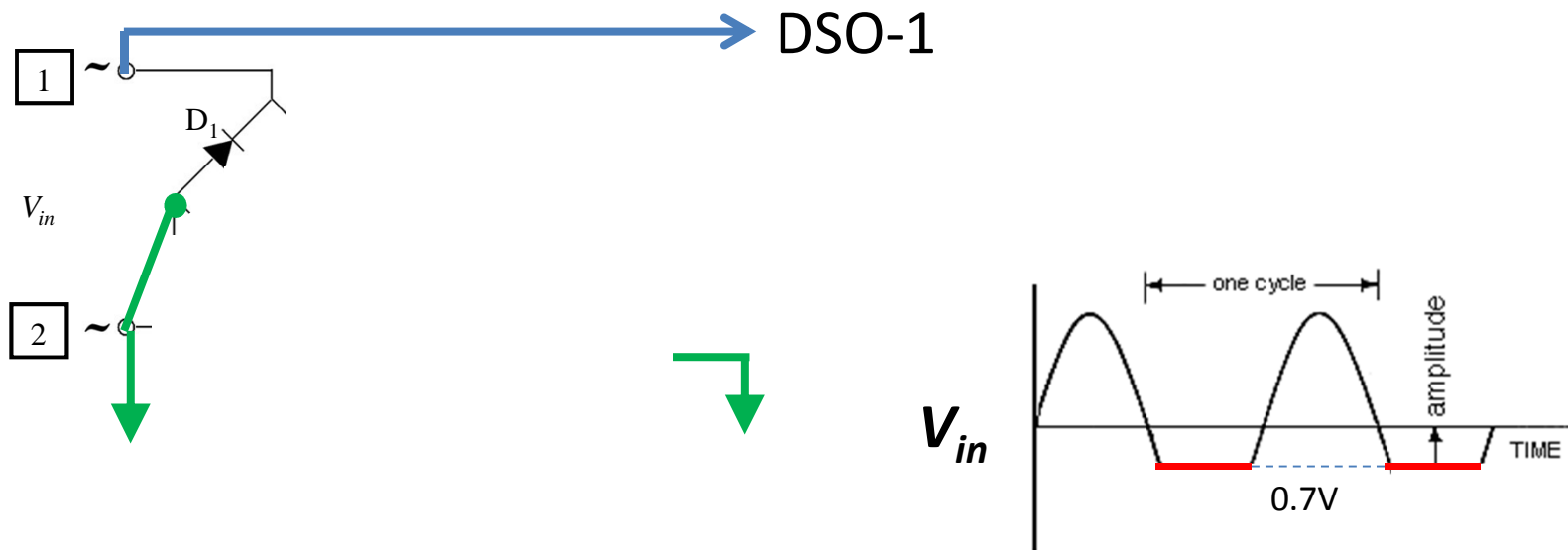
# Full wave rectifier

Looks like a negative clamp from  $V_{in}$

<http://www.falstad.com/circuit/e-fullrect.html>





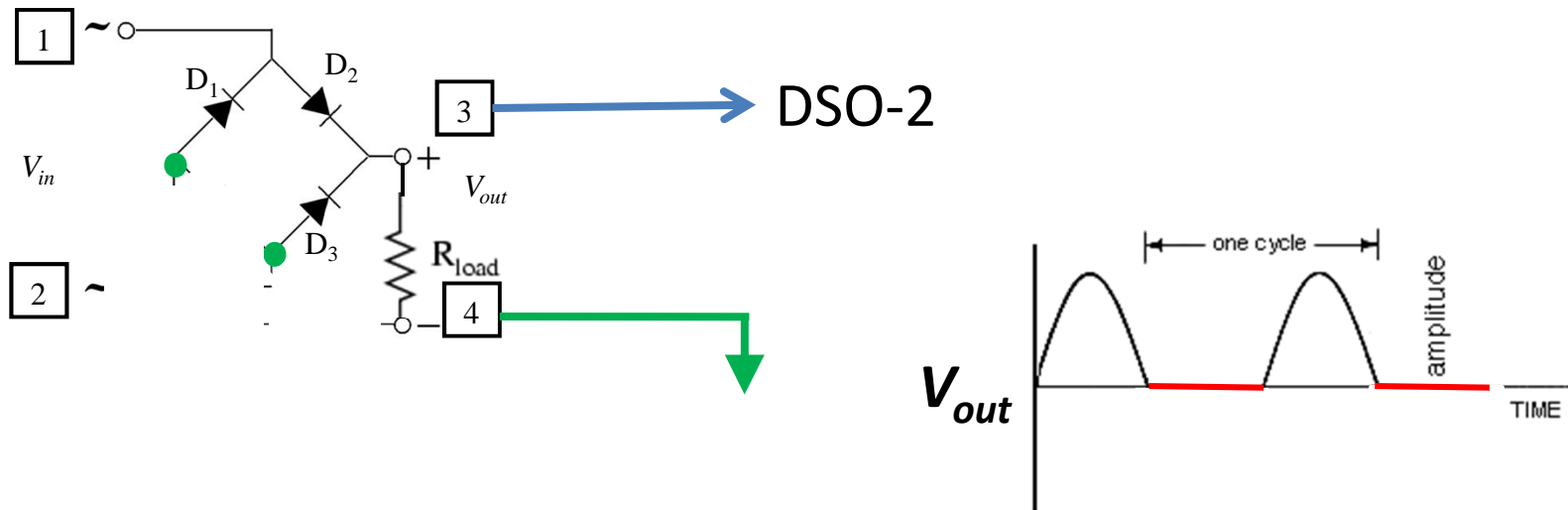
# Full wave rectifier

Looks like a half-wave rectifier from  $V_{out}$

<http://www.falstad.com/circuit/e-fullrect.html>





Note:  $D_1$  and  $D_3$  function as positive clamps (like Slide 4)  
– but are irrelevant, because the half-wave rectification makes sure that  $V_{out}$  is always positive.
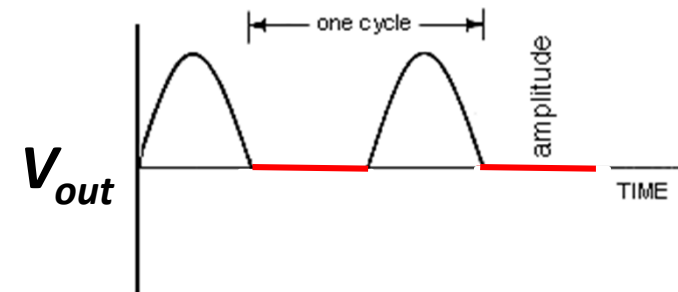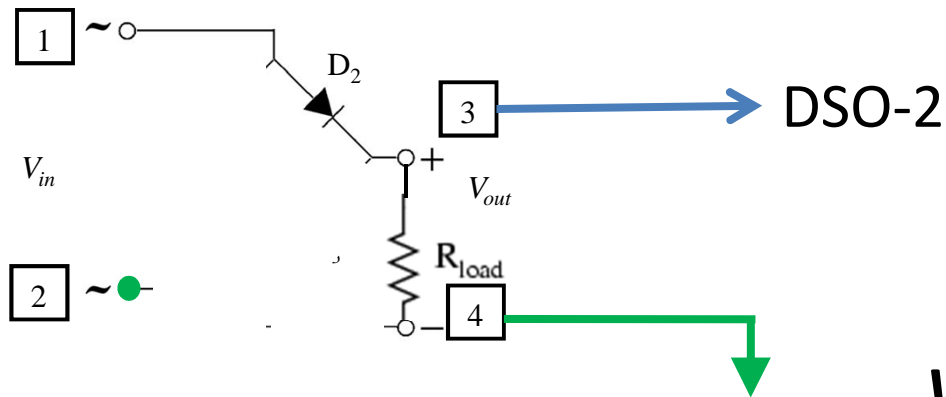
# Full wave rectifier

Looks like a half-wave rectifier from  $V_{out}$

<http://www.falstad.com/circuit/e-fullrect.html>



Notice the green dots which represent 0V



# Prep for Lab 3

We have used 'working' definitions of Diode operation:

Cathode to Anode voltage  $> 0.7V \rightarrow$  'ON'

Cathode to Anode voltage  $< 0.7V \rightarrow$  'OFF'

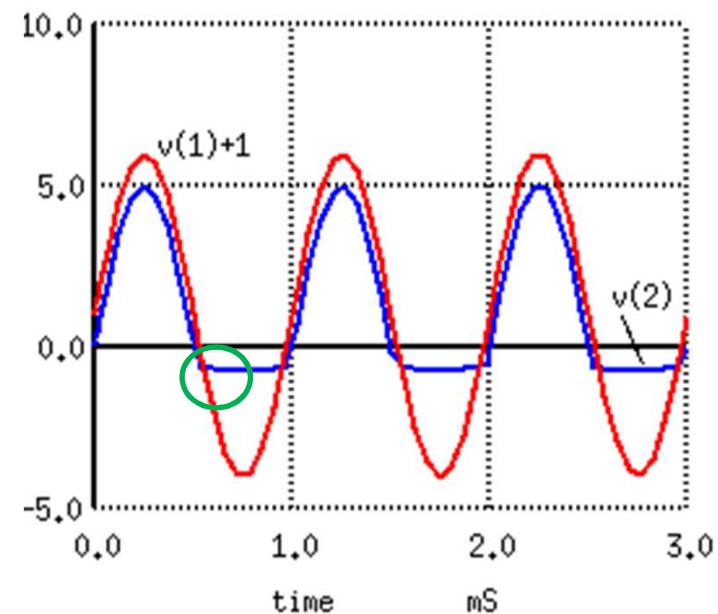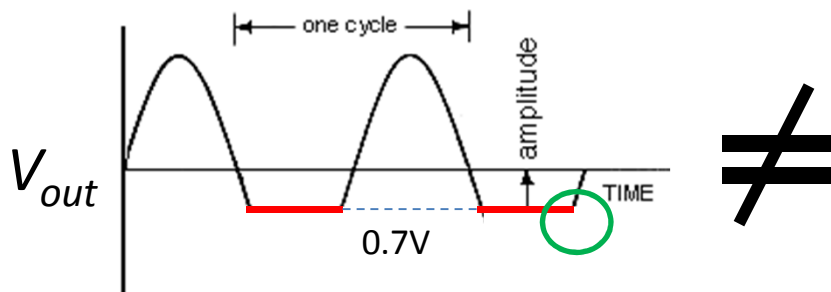This is not good enough for detailed circuit building & analysis



# I-V characteristics of two terminal devices

---

As the voltage across a diode increases from 0.65V to 0.75V  
it changes smoothly from: (V)

- A state of not conducting current (I)
- To a state of conducting current

We will learn how to determine the **I-V** characteristics of any two terminal device without using graph paper!

# Useful reference for this course

---

“Foundations of Analog and Digital Electronics”  
by Anant Agarwal and Jeffrey Lang

<http://www.allaboutcircuits.com>