

EP215

Electronics Lab 1

Lecture 4

Review of Lab 3: I-V characteristics
and stray effects

What is special about the differential input test setup?

 


Fig 1: Setup for Assignment 3

Input signal at these points
Must not refer to **GND** potential

What is special about the differential input test setup?

 


Fig 1: Setup for Assignment 3

If one leg of the signal is GND,
No current across R_{ref} !


Lab 3: I-V characteristics

<http://www.falstad.com/circuit/e-diodecurve.html>




Diode I-V at low frequency


PN junction

 


Reverse Bias

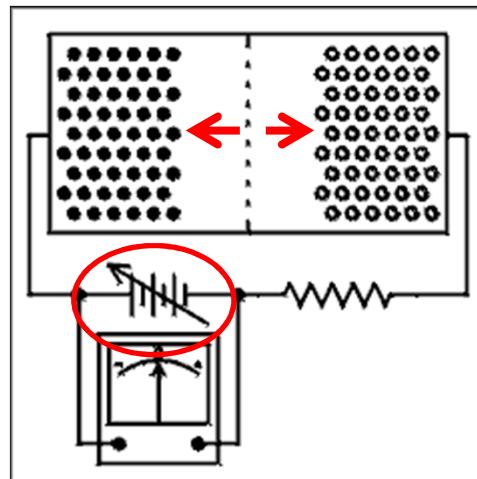



Forward Bias

 

Bound charge between
metal electrodes
→ Capacitor

 


Diode I-V at low frequency

  

Diode I-V at high frequency

 
Effective capacitance of the depletion layer becomes important at high frequency



$$r_D \approx \frac{nV_T}{I_D}$$

$$C_d = \frac{\tau_T \cdot I_D}{V_T}$$

 
Forward bias: $\begin{cases} C_j \approx 2 \cdot C_{j0} \\ C_d = \frac{\tau_T \cdot I_D}{V_T} \end{cases}$ Reverse bias: $\begin{cases} C_j = \frac{C_{j0}}{\left(1 - \frac{V_D}{V_0}\right)^m} \\ C_d = 0 \end{cases}$



Note:
in dimension:
time * current = charge
So $C = Q/V$ makes sense

Diode I-V at high frequency

 Different capacitance in Forward and Reverse bias:




Different transit times of charge across the depletion barrier

→ r_d and $(C_j + C_d)$ determine a time constant



→ As frequency of V_{in} changes, the time constant causes delayed response.

Resistor I-V characteristics

 


This schematic works fine at low frequency when the resistor behaves like an 'ideal' resistor.

 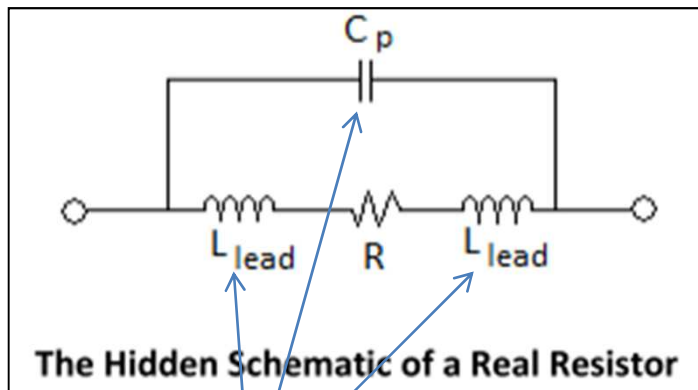In reality, there is a 'hidden' schematic behind every device




 Note: these are parasitic, frequency dependent effective components of very small value.
So there is no infinite loop here!



See accompanying notes on 'The Hidden Schematic'

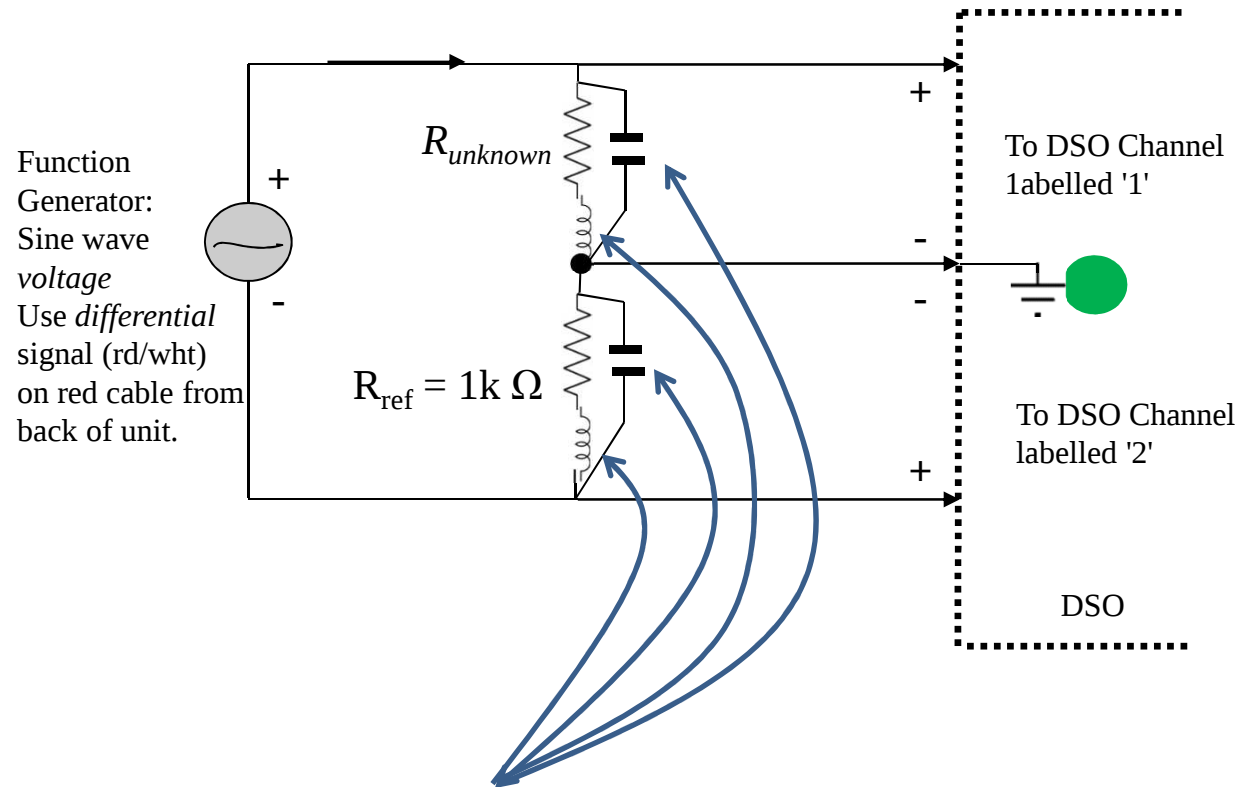
At high frequency, our test setup changes




All these parasitic component values are different

What is the effect of parasitic components on I-V characteristic?

 
What do V and I look like in the time domain?



Resistor: $V_R = R * I_R$

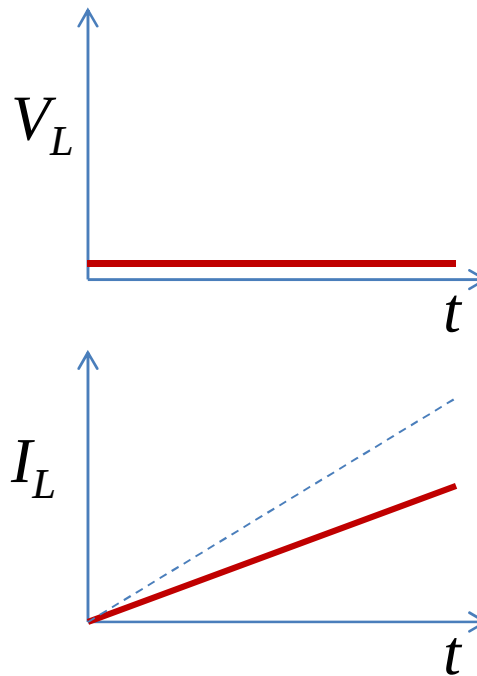

 
L: $V_L = L * dI_L / dt$
Small L is in series,
so $I_L = I_R$ linear



C: $V_C = C * \int I dt$
 C in parallel, gets
very small I from I_R

What is the effect of parasitic components on I-V characteristic?

 In our cool X-Y display format to get I-V characteristics:



Resistor: $V_R = R * I_R$


C: $V_L = C * \int I dt$
*C in parallel, gets
very small I from I_R*

What's next?


Transistor

Bipolar junction transistor

 Graduating from a two terminal device to a three terminal device



NPN transistor

 

Base-Emitter junction
diode highlighted as ' r_e '