
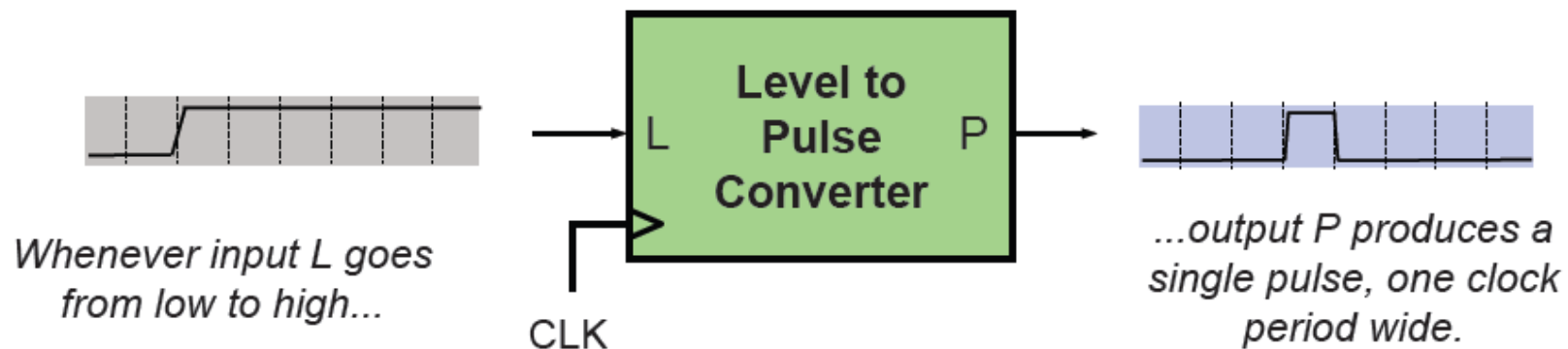


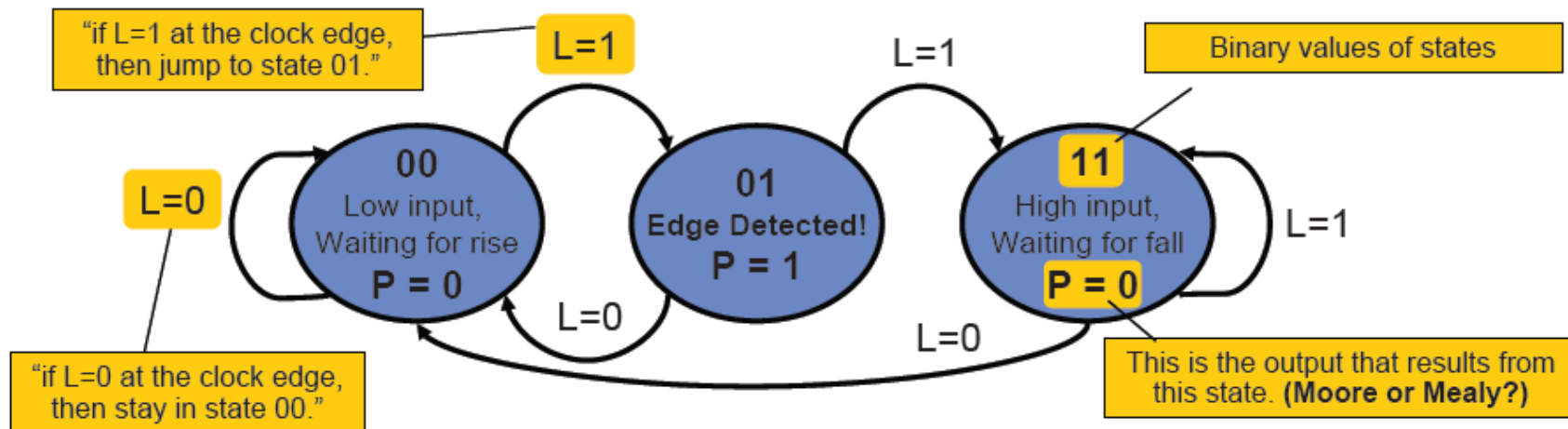- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- In other words, it's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters




- **State transition diagram** is a useful FSM representation and design aid




Logic Derivation for a Moore FSM

 - Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

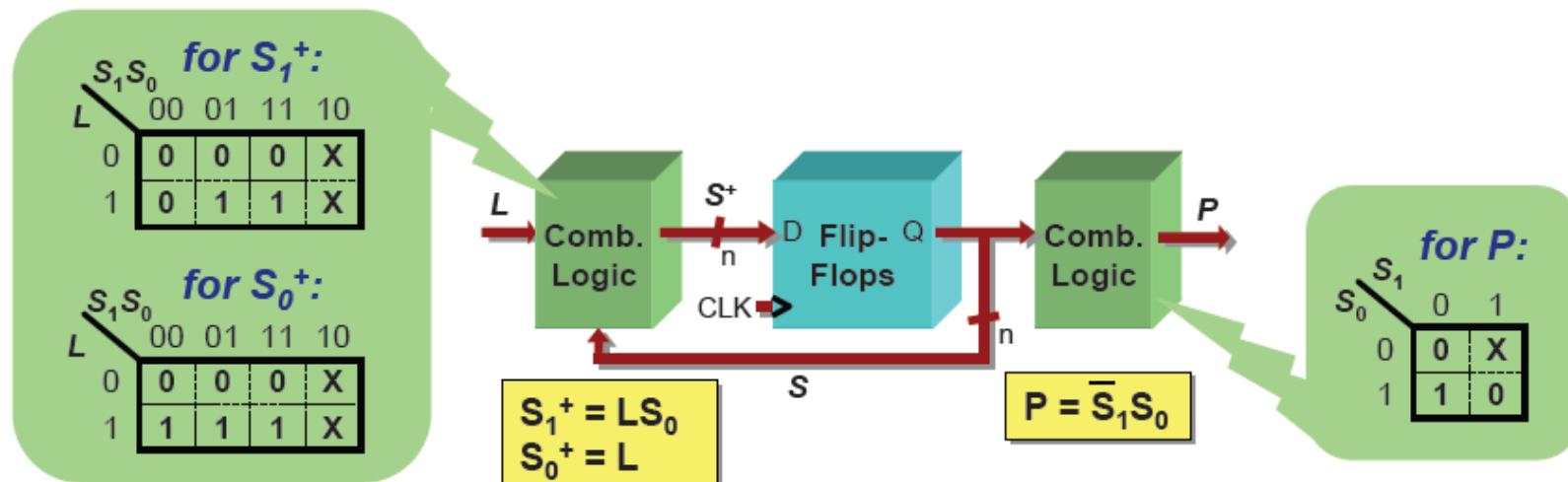
- Combinational logic may be derived by Karnaugh maps



Moore Implementation

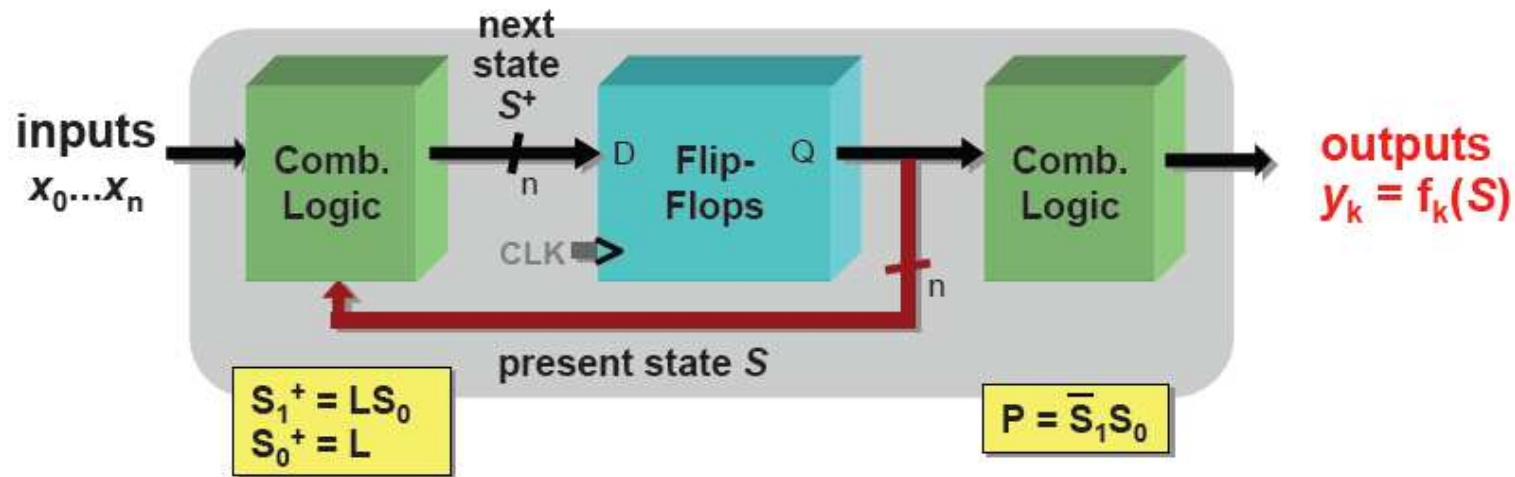


 Moore FSM circuit implementation of level-to-pulse converter:




Note: 3 states, so $2^2 = 4 > 3$ i.e. 2 memory bits needed, with one unused state

Mealy FSM Design

 


Pres. State	In	Next State	Out
S	L	S^+	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

 Mealy FSM circuit implementation of level-to-pulse converter:




- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions

Mealy FSM implementation

 

 
- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




Mealy/Moore FSM Trade-Offs

- Remember that the difference is in the output:
 - Moore outputs are based on state only
 - Mealy outputs are based on state *and input*
 - Therefore, Mealy outputs generally occur one cycle earlier than a Moore:

Moore: delayed assertion of P

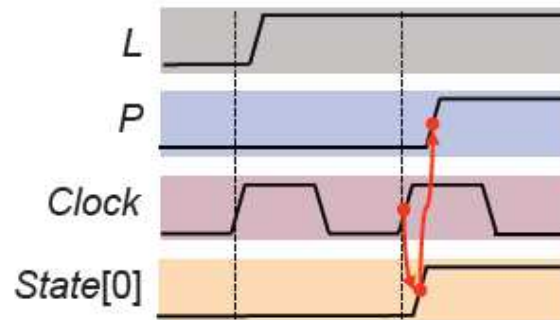

Mealy: immediate assertion of P

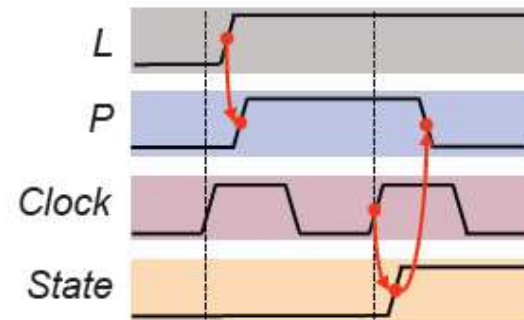

- Compared to a Moore FSM, a Mealy FSM might...
 - Be more difficult to conceptualize and design
 - Have fewer states