

## Laboratory 7 – Digital to Analog Converter

### Procedure:

This assignment has a single Exercise with several Questions. Work out the solution to the design problem first on paper and implement it on a breadboard. You are required to submit the complete question and answer sheet with your design and answers filled in where asked, and show your working circuit to a TA.

### Designing a Digital-to-Analog Converter:

#### Introduction:

A Digital-to-Analog Converter (DAC) converts a digital input code into an analog output voltage. It takes a digital input signal as an  $n$ -bit number represented by TTL logic levels, and produces a proportional analog output voltage in a fixed range. For example, a 4-bit parallel DAC would have four input lines, and have an input range corresponding to (0000-1111) (0-15). If we fix the analog output voltage range of this DAC to be 0 V to 4 V, then any input code between 0000 and 1111 would give a proportionally intermediate value of output voltage, as shown in Fig. 1. The larger, the number of bits, the smaller the 'step size' in Fig 1 – i.e. the response of the DAC suffers from lesser *quantization* error as you increase the number of bits.

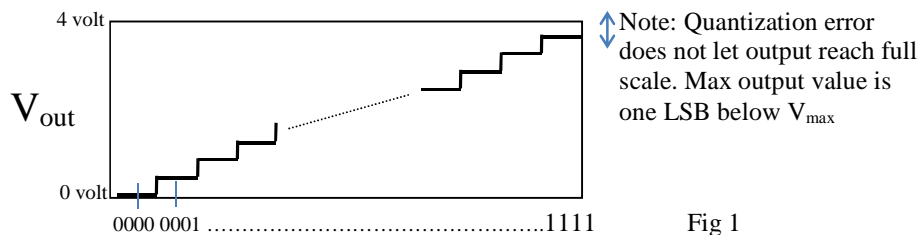


Fig 1

There are many different types of DAC's – the designs have different trade-offs between linearity, speed of conversion, output drive capability etc. We will design and analyze a very basic DAC.

### Problem Statement:

Design a 4-bit DAC using the following parameters:

- It must have only passive components. Note that passive components  $\rightarrow$  R,L,C. Of these, R is the only *linear* passive – and linearity is a desirable property of a DAC as seen in Fig 1. So we will build our DAC using resistors. In particular, we will use only two values of resistors.
- The DAC's output voltage is controlled by a combination of 4 digital bits:  $\text{Bit}_3\text{Bit}_2\text{Bit}_1\text{Bit}_0$
- The analog voltage range of the DAC must be set externally.

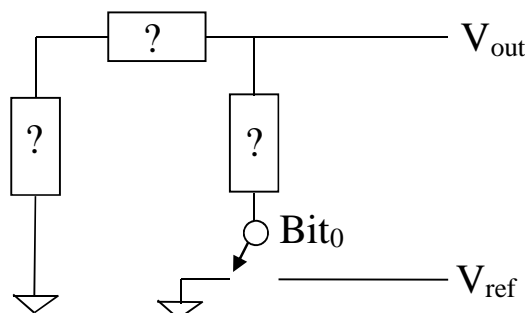


Fig 1: Simple 1-bit DAC.  
Design a 1-bit DAC  
Controlled by  $\text{Bit}_0$   
[Questions 1-4]

Name:

Roll #

Questions 1 to 4 refer to Fig 1 as the simple starting point of your design

1: What are the components you would put in the blocks marked with a '?', and what are their values, relative to each other? Do the actual values of the components matter?

/1

2: Work out the equation that determines  $V_{\text{out}}$  as a function of  $\text{Bit}_0$ ,  $V_{\text{max}}$  and the component values you have set for the 1-bit DAC.

/1

3.1: What is the maximum output voltage of the DAC?  
How would you change the maximum output voltage?

/1

3.2: What is the minimum value of the DAC output voltage?  
How would you change the minimum output voltage?

/1

4: What is the output impedance of this circuit? What restrictions does it place it on the load?

/2

5: Now extend your design from a 1-bit DAC into a 4-bit DAC. Draw the DAC design below with the appropriate component values filled in, and work out the full equation for the 4-bit DAC as in Question 2  
*Hint:* You are only allowed to use two values of components.

/7

6: Wire up the DAC on a breadboard using any suitable component values. Demonstrate its operation to a TA with three or four suitable inputs from the 0000-1111 range. Use wires connected to  $V_{\text{min}}$  or  $V_{\text{max}}$  as Switches representing  $B_3B_2B_1B_0$ . Be neat!  
It should be possible for us to understand your circuit design by simple inspection.  
Leave the circuit connected on your breadboard for future use.

/2

7: Although we have used the term 'voltage' in all the above questions,  
Is the output of the DAC a voltage output or a current output?

/1 bonus

Total: /15+1