

Name: \_\_\_\_\_

Roll Number: \_\_\_\_\_

## Laboratory 8


A:	/4	B:	/3	C:	/3	D:	/5	Tot:	/15
----	----	----	----	----	----	----	----	------	-----

### Relaxation Oscillators

This lab consists of three modules. We will see how parasitic effects can occasionally be used to a designer's advantage

#### Part A: Capacitor in feedback loop

Fig 1:  $C_f$  in feedback loop.

 

Consider the circuit of Fig 1. Notice the difference from standard inverting feedback amplifier: the feedback resistor has been replaced by a capacitor  $C_f$ .

Consider the mathematics below and choose the *correct* type of capacitor  $C_f$  (electrolytic or non-polar)

**C must be non-polar polystyrene signal cap**

**Q1:** Calculate the *time-domain* response of  $V_{out}$  to  $V_{in}$ . We have generally calculated the gain of such feedback circuits as  $(1+Z_f/Z_s)$  where  $Z_f$  and  $Z_s$  are the impedances in the feedback and source connections. The time-domain response requires you to apply the golden rules of opamp design *and* the current-voltage relationship for a capacitor  $I = C \, dV/dt$  followed by some algebra.

**Current at (-) input :  $V_{in}/R + C \, dV_o/dt = 0$  so  $V_o = -1/RC \int V_{in} dt \rightarrow$  Integrator (with - sign)**

/1

**Q2:** Choose suitable values of the passive components  $R_s$ ,  $C_f$  such that the time constant of your design is 1 ms.

/1

**Q3:** Build the circuit of Fig 1 and drive it with a *square*  $V_{in}$  of amplitude 2V peak-to-peak. Draw a diagram of your observations here and verify that your calculations of Q1 above are correct.

**Square integration  $\rightarrow$  triangular waveform**

/1


**Q4:** Set  $V_{in}=0$  by grounding it. Turn off supply to the circuit. When you turn the supply back on, observe the trace of  $V_{out}$  on a long time scale  $\sim 1$  sec on the DSO. Record your observations here, and state a possible hypothesis for the observed behavior

**Small internal input offset voltage of opamp ( $V_{os}$ ) is integrated until the output saturates**

/1

Name: \_\_\_\_\_

Roll Number: \_\_\_\_\_

 **Part B: Capacitor connected at Input**Fig 2:  $C_s$  at source

Consider the circuit of Fig 2. Notice the difference from standard inverting feedback amplifier: the *source* resistor has been replaced by a capacitor  $C_s$ .

**Q1:** Calculate the *time-domain* response of  $V_{out}$  to  $V_{in}$  as in Part A. The time-domain response requires you to apply the golden rules of opamp design *and* the current-voltage relationship for a capacitor  $I = C \frac{dV}{dt}$  followed by some algebra.

Current at (-) input :  $V_o/R + C \frac{dV_{in}}{dt} = 0$  so  $V_o = -RC \frac{dV_{in}}{dt}$  → Differentiator (with - sign)

/1

**Q2:** Choose suitable values of the passive components  $R_s, C_f$  such that the time constant of your design is 1 ms.

/1

**Q3:** Build the circuit of Fig 2 and drive it with a *square*  $V_{in}$  of amplitude 2V peak-to-peak. Draw a diagram of your observations here and verify that your calculations of Q1 above are correct.

Square differentiate → flat 0 except +/- delta functions at edges

/1

Name: \_\_\_\_\_

Roll Number: \_\_\_\_\_

**Part C: Comparator**

Recall the simple comparator (with Hysteresis) circuit using positive feedback we studied earlier in Lab 2. The function of a comparator is to feedback a fraction of  $V_{out}$  to the (+) input so that when  $V_{in}$  exceeds a threshold set by the feedback fraction  $R_f^+/R^+$ , the output switches to  $-V_{sat}$  and when  $V_{in}$  falls below threshold, output switches to  $+V_{sat}$ .

Use your memory/logic and draw the diagram of a simple comparator circuit here, with  $V_{in} = 0$

 


Fig 3: Simple comparator with positive feedback. Set the reference voltage for comparison to  $V_{sat} * (R^+ / (R_f^+ + R^+))$

/0.25

In view of your measurements in Part A and Part B:

**Q1:** Predict the value of  $V_{out}$  in your circuit with  $V_{in} = 0$ :

- a) What is  $V_{out}$  at  $t=0$  immediately when the circuit is turned on?  $0V$
- b) What is  $V_{out}$  in the very short time  $\sim$  microseconds after the circuit is turned on?
- c) What is  $V_{out}$  in steady state after the circuit has been on for a few seconds:  $\pm V_{sat}$

/0.5

/0.5

/0.25

**Q2:** Connect up the circuit you have designed in Fig 3 and *demonstrate* the validity of your predictions

Use this space to record your DSO observations of  $V_{out}$  in detail. Note that  $V_{in} = 0$  for a), b), c)

/1.5

Name: \_\_\_\_\_

Roll Number: \_\_\_\_\_

**Part D: Relaxation oscillator**

Use your observations and conclusions from Parts A, B and C to make an opamp circuit that demonstrates the following behavior:

1. It's  $V_{out}$  oscillates between  $+V_{sat}$  and  $-V_{sat}$
2. It has no external  $V_{in}$  applied
3. The oscillation time period is 1 ms

Hint: You will need to use Part C and any one of Parts A or B

Draw your circuit design here. Calculate and mark the value of the components required.

Comparator with differentiator in negative feedback loop

Relies on delta function created by 0 to  $+V_{sat}$  switching to force output to switch to  $-V_{sat}$  and vice-versa

/2.5

/2.5

This type of oscillator is called a 'Relaxation Oscillator'. Build your circuit and demonstrate its operation